
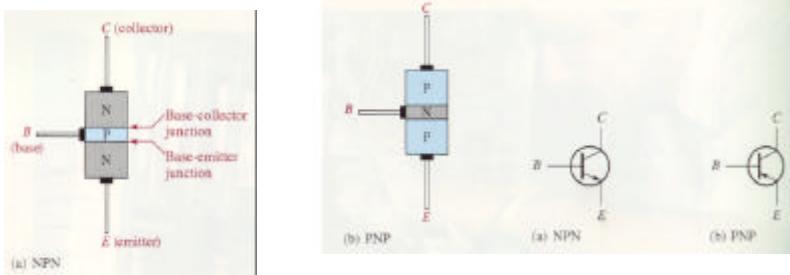


BIPOLAR JUNCTION TRANSISTORS


- Two junction, three terminal device

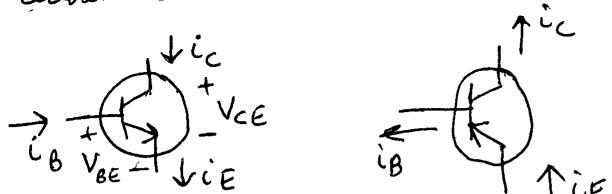


- Current Directions and Voltage



NPN

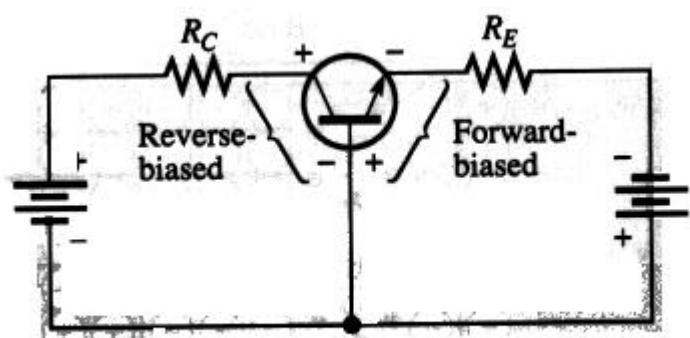


(a) NPN

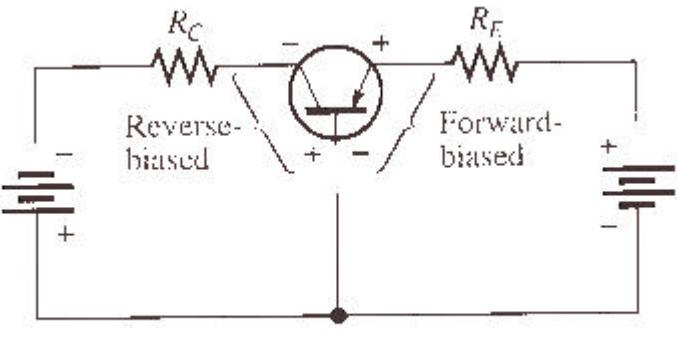


(b) PNP


<i>Condition</i>	<i>E-B Junction</i>	<i>C-B Junction</i>	<i>Region of Operation</i>
I	Forward biased	Reverse (or un-) biased	Active
II	Forward biased	Forward biased	Saturation
III	Reverse biased	Reverse (or un-) biased	Cutoff
IV	Reverse biased	Forward biased	Inverted

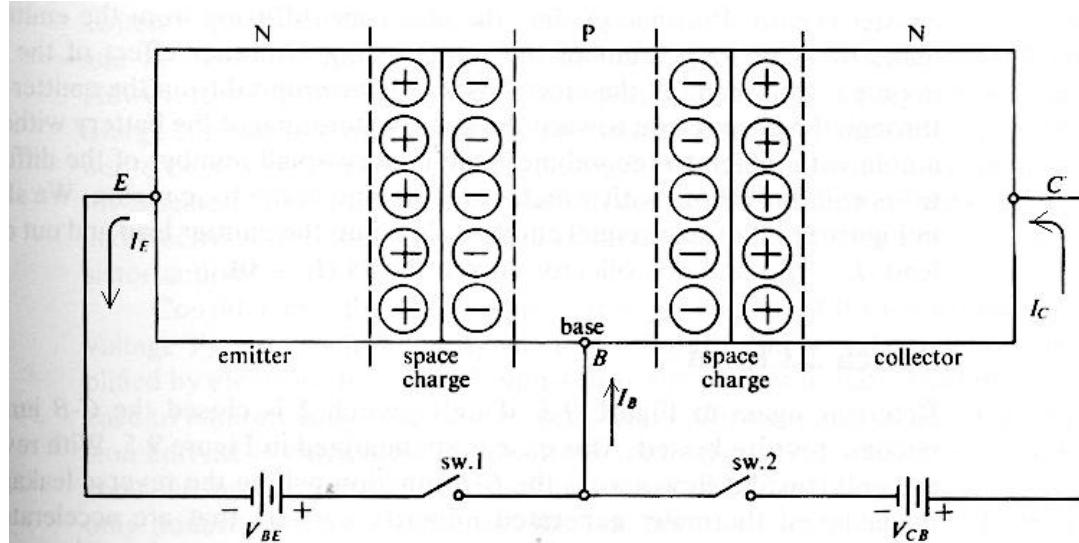

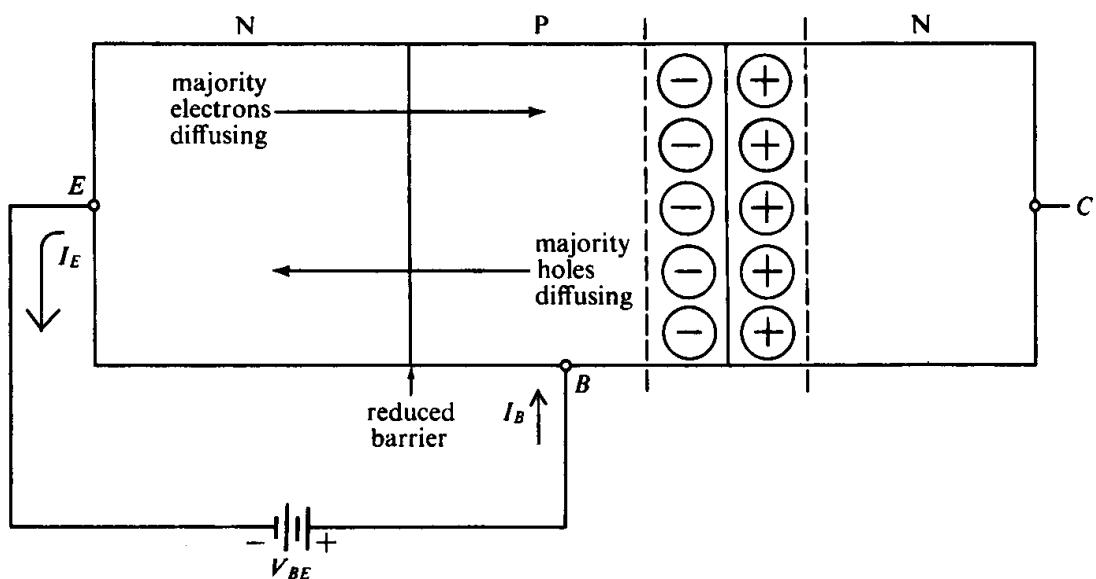
Biasing the NPN transistor for active operation



Switch 1 closed, switch 2 open

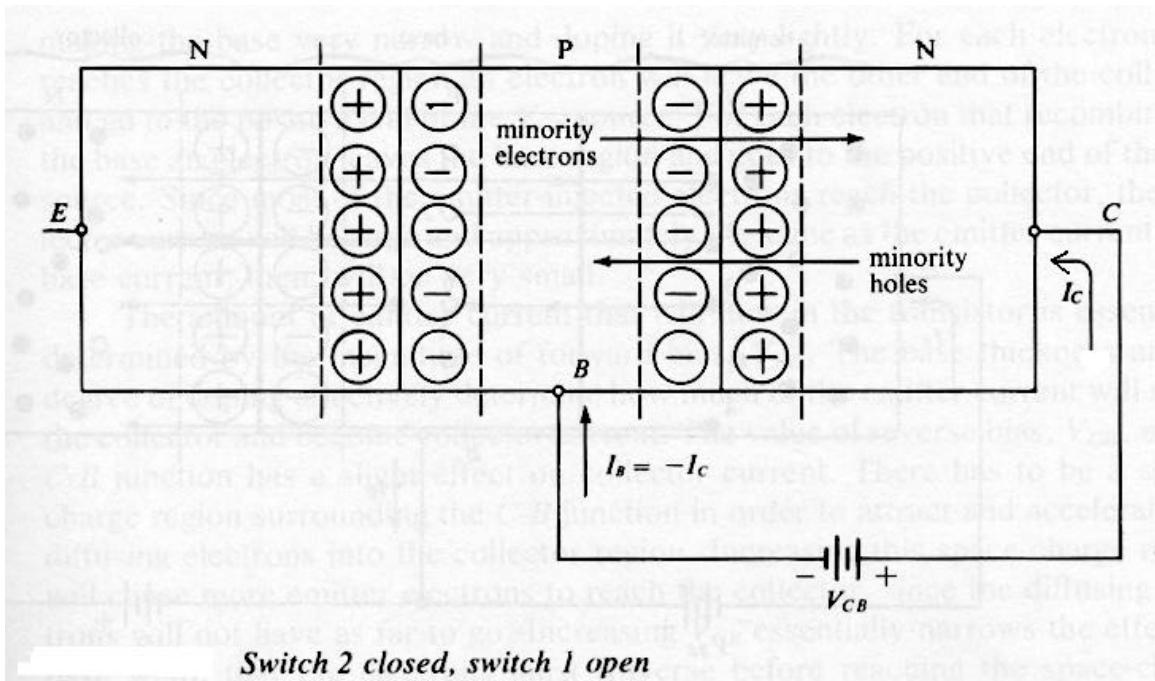


Switch 2 closed, switch 1 open

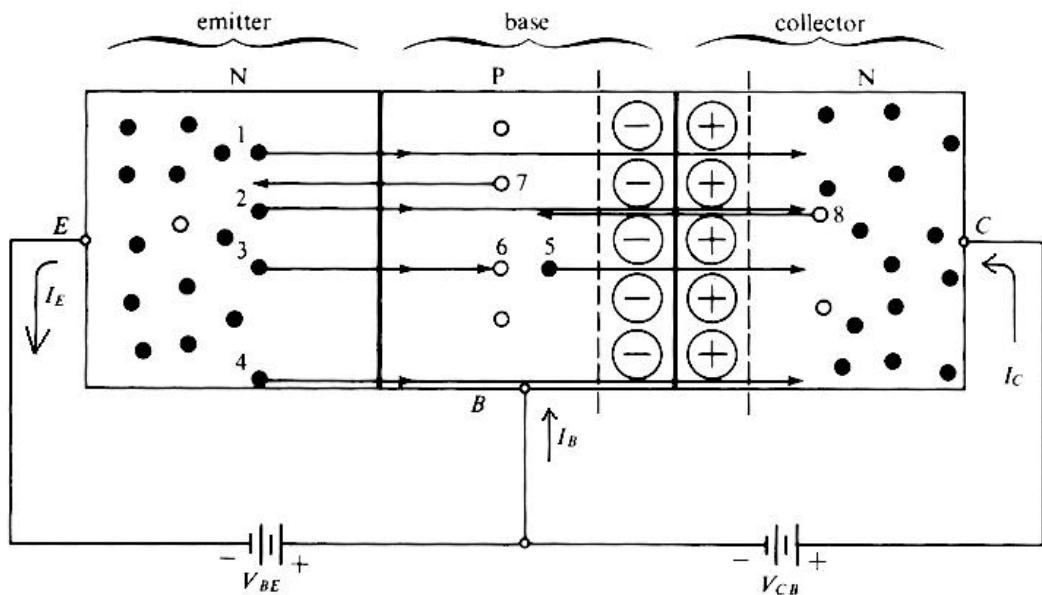

Switch 1 and switch 2 closed; NPN transistor operating in the active region


Operating Regions

Active:

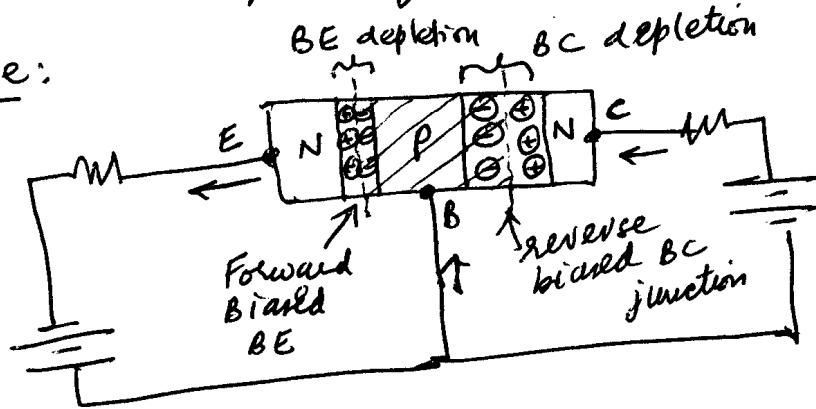


- Base region lightly doped
 - Base region is thin
- To have mostly electron flow and also have through flow.

Saturation:

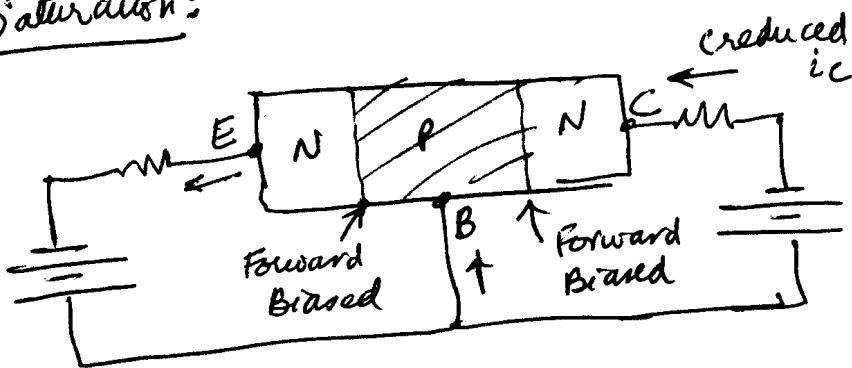

Cutoff:

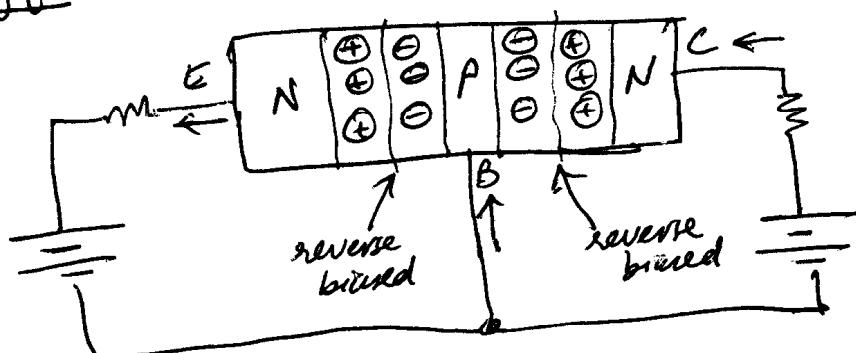


(reverse biased or open)

$$i_B = 0 \Rightarrow i_C = 0$$

Transistor Currents.



NPN

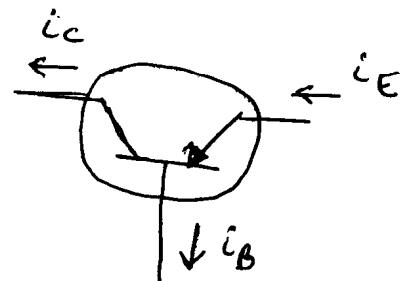

PNP

$$i_E = i_C + i_B \quad \text{--- (1)}$$

$$i_C = \alpha i_E \quad \text{--- (2)}$$

$$i_C = \beta i_B \quad \text{--- (3)}$$


Using (1), (2) and (3)

$$\beta = \frac{\alpha}{1 - \alpha}$$

SHOCKLEY

$$i_E = I_{ES} \left[\exp\left(\frac{v_{BE}}{V_T}\right) - 1 \right] \quad \text{--- (4)}$$

Same as diode equation with $n = 1$

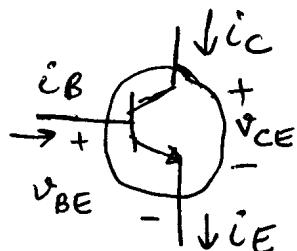

Because of (2), we get


$$i_C = \alpha I_{ES} \left[\exp\left(\frac{v_{BE}}{V_T}\right) - 1 \right] \quad \text{--- (5)}$$

From (1) & (2) $i_B = (1 - \alpha) i_E \quad \text{--- (6)}$

Using (4) in (6), we get

$$i_B = (1 - \alpha) I_{ES} \left[\exp\left(\frac{v_{BE}}{V_T}\right) - 1 \right]$$

PNP currents

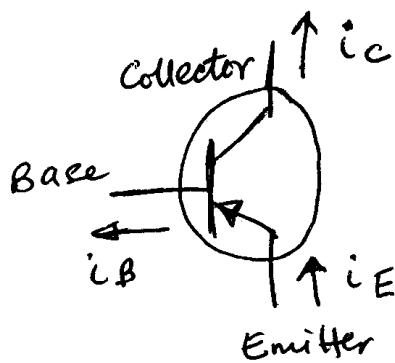


PNP

For Shockley equations,
replace V_{BE} with $-V_{BE}$.

For example

$$i_E = I_{ES} \left[\exp\left(\frac{-V_{BE}}{V_T}\right) - 1 \right]$$


Common Emitter Characteristics

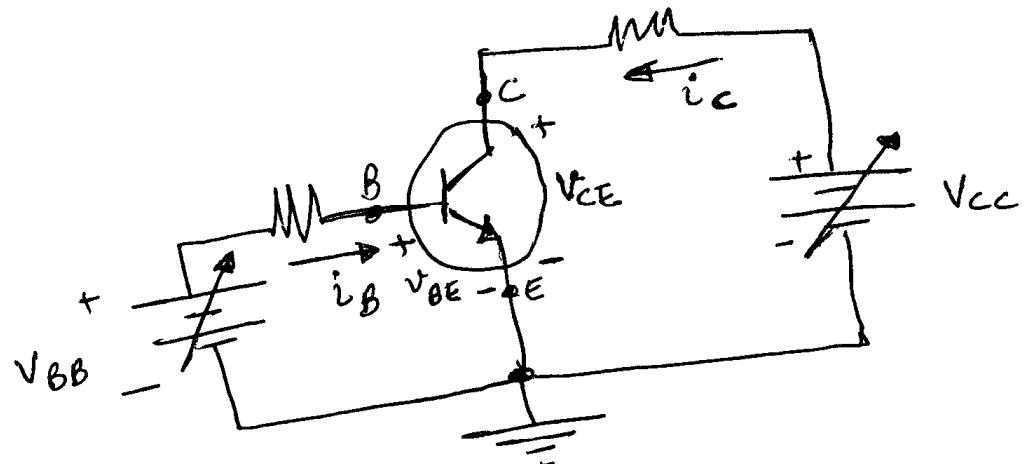


$$V_{BC} = V_{BE} - V_{CE}$$

For V_{BC} to be negative (to produce reverse biased EB junction), we need $V_{CE} > V_{BE}$.

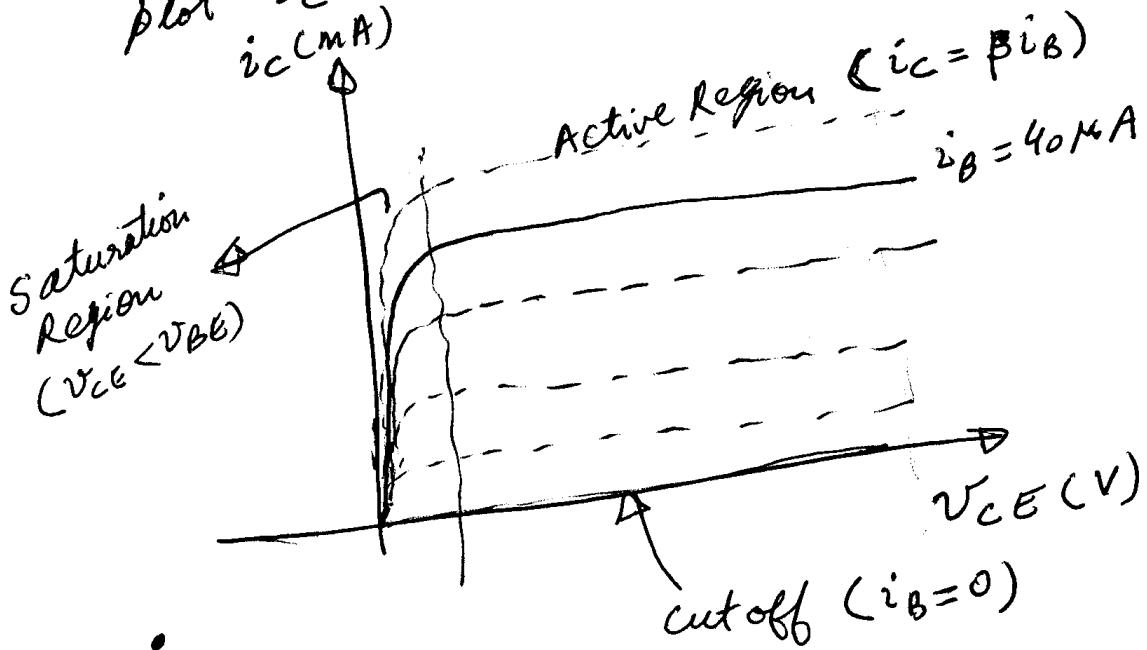
- Fix i_B by fixing V_{BB} , then vary V_{CC} to plot i_C versus V_{CE} for a constant i_B .



Input Characteristics

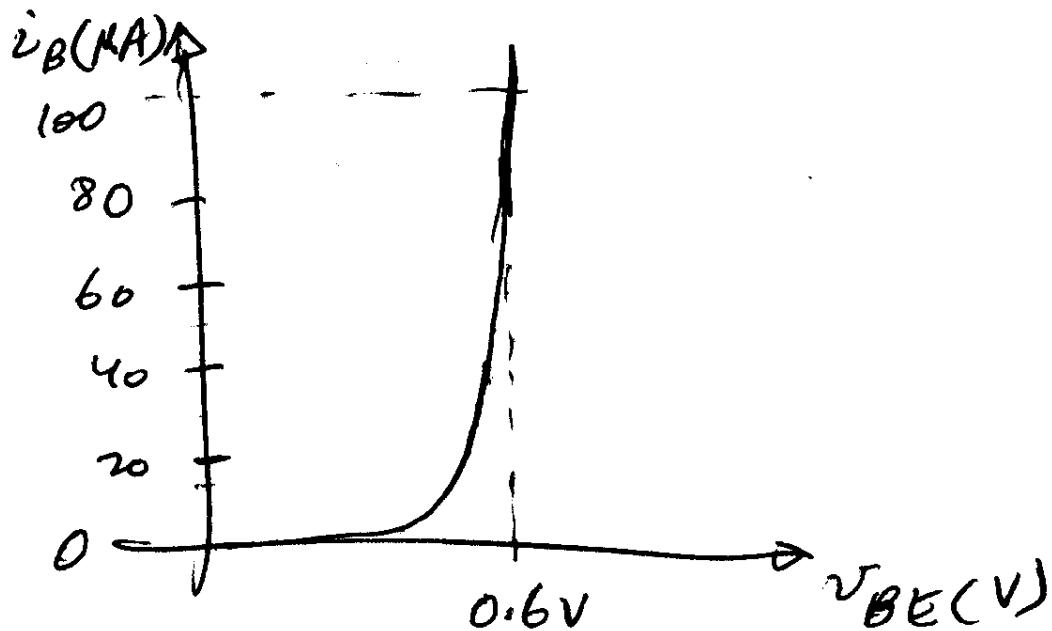

Output Characteristics

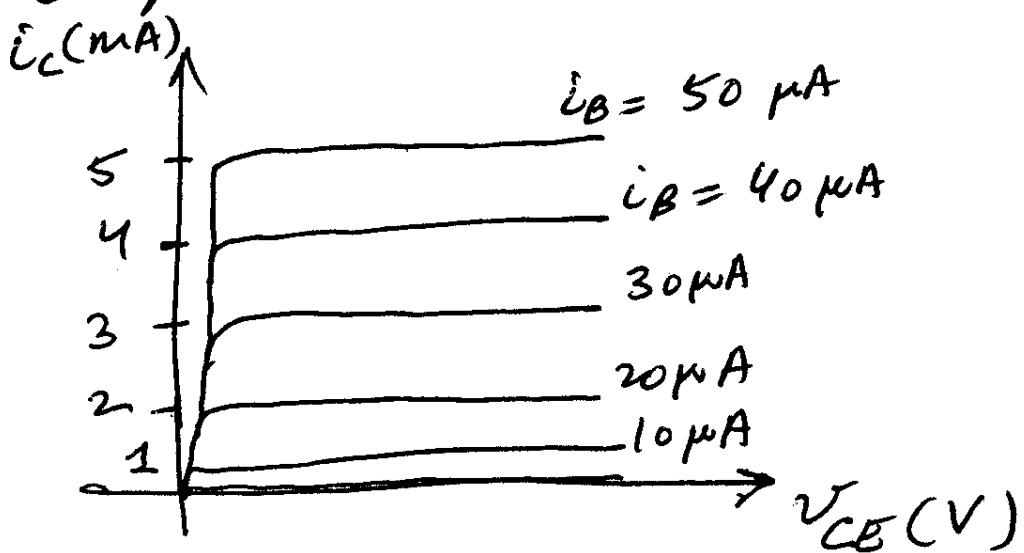


$$\text{Amplification } i_C = \beta i_B$$


$$\beta = \frac{5 \text{ mA}}{50 \mu \text{A}} = 100$$

$$\beta_{ac} = \frac{\Delta i_C}{\Delta i_B} = \frac{5 \text{ mA}}{10 \mu \text{A}} = 100$$

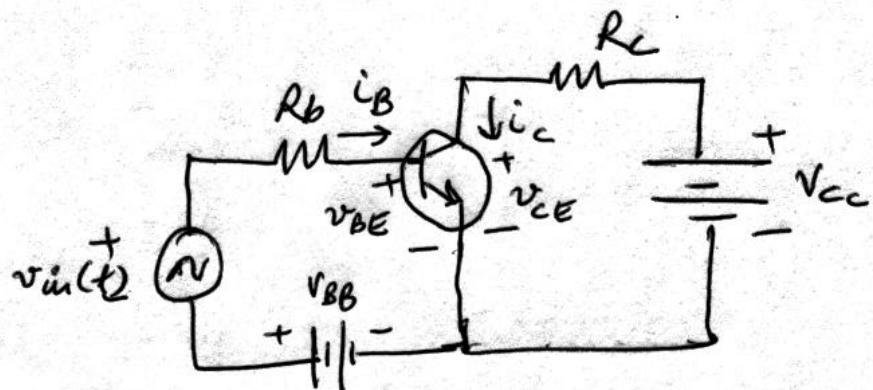Load-line Analysis of a Common-Emitter Amplifier




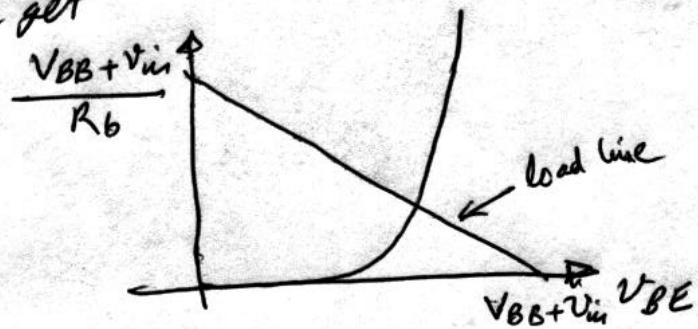using KVL in left loop, we get $V_{BB} + v_{in}(t) = R_B i_B(t) + v_{BE}(t)$ —①




Output circuit

$$V_{CC} = i_C R_C + V_{CE}$$

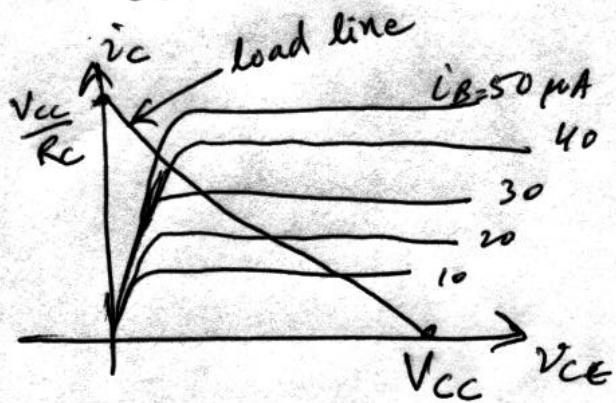

EXAMPLE:

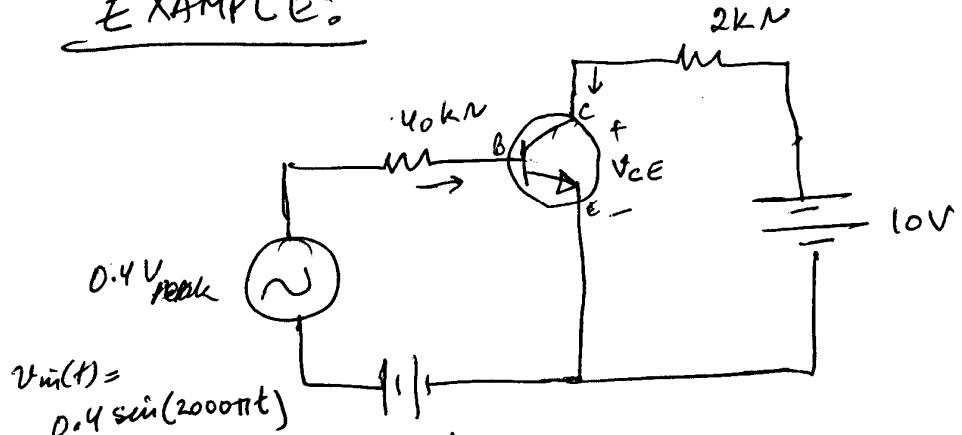

$$v_{in}(t) = 0.4 \sin(2000\pi t)$$

INPUT EQUATION

For
\$v_{in} = 0\$

$$v_{BB} + v_{in} = R_B i_B + v_{BE}$$

$$1.6 + v_{in}^0 = 40,000 i_B + v_{BE}$$

$$\text{when } i_B = 0 \Rightarrow v_{BE} = 1.6V$$

$$\text{if } v_{BE} = 0 \Rightarrow i_B = 40 \mu A$$



For
Point ①, \$i_B = 25 \mu A\$, ② \$i_B = 35 \mu A\$
③, \$i_B = 15 \mu A\$

OUTPUT EQUATION

$$v_{CE} = R_C i_C + v_{CE}$$

$$\text{when } i_C = 0 \Rightarrow v_{CE} = V_{CC} = 10$$
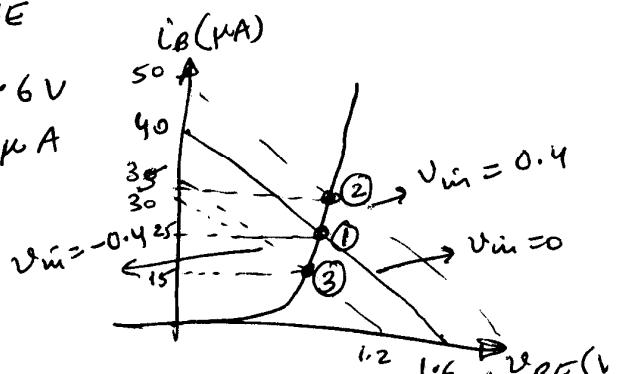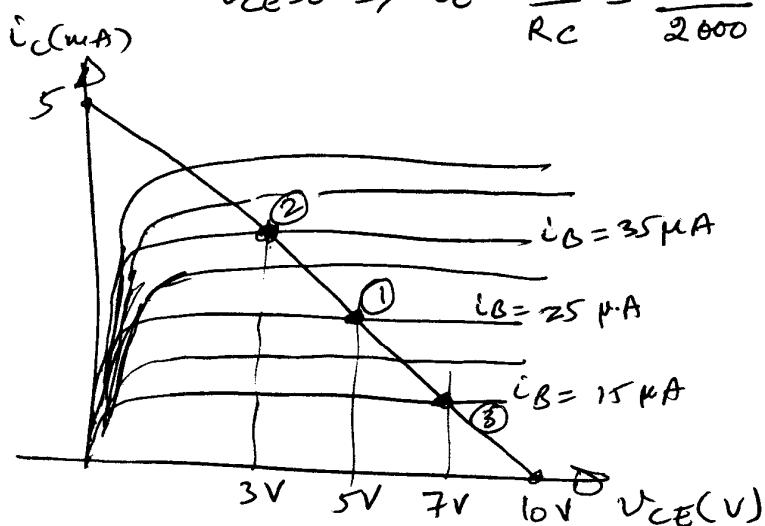
$$\text{if } v_{CE} = 0 \Rightarrow i_C = \frac{V_{CC}}{R_C} = \frac{10}{2000} \text{ Amps} = 5 \text{ mA.}$$



Peak to Peak input voltage = \$0.8V\$

" " " output " = \$4V\$

$$\therefore \boxed{\text{Voltage gain} = \frac{4}{0.8} = 5} = -5 \text{ +ve sign showing signal inversion}$$

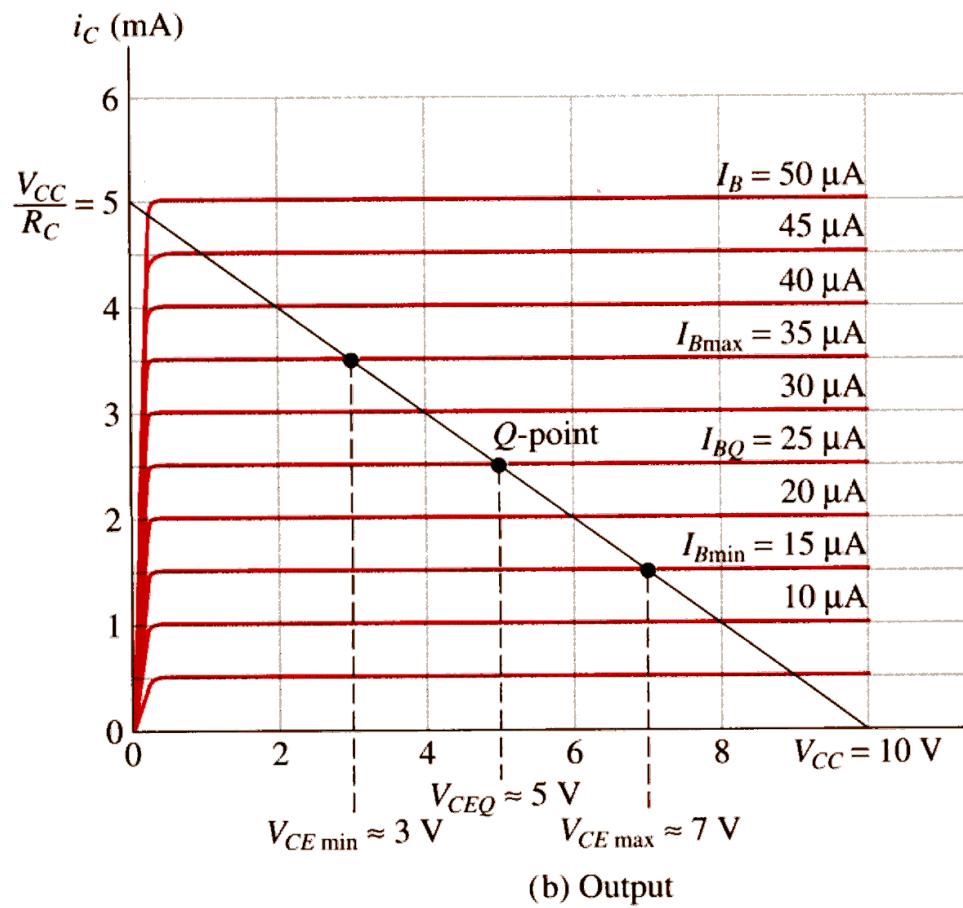
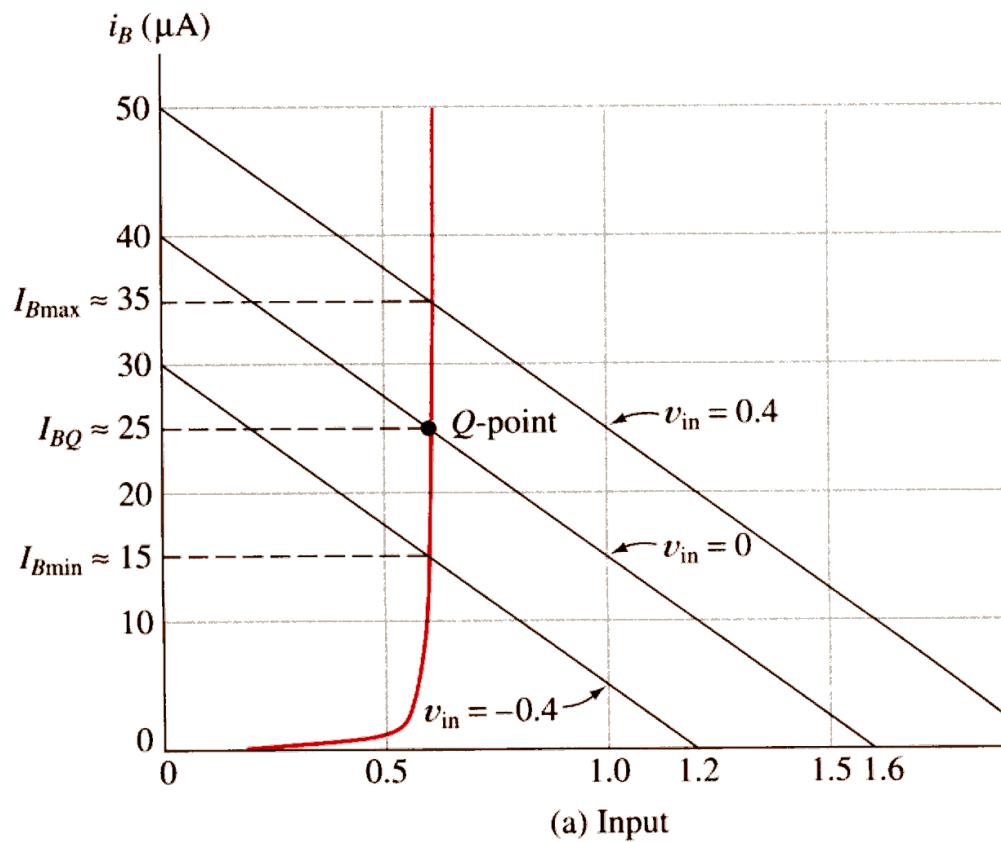


Figure 5.9 Load-line analysis for Example 5.2.


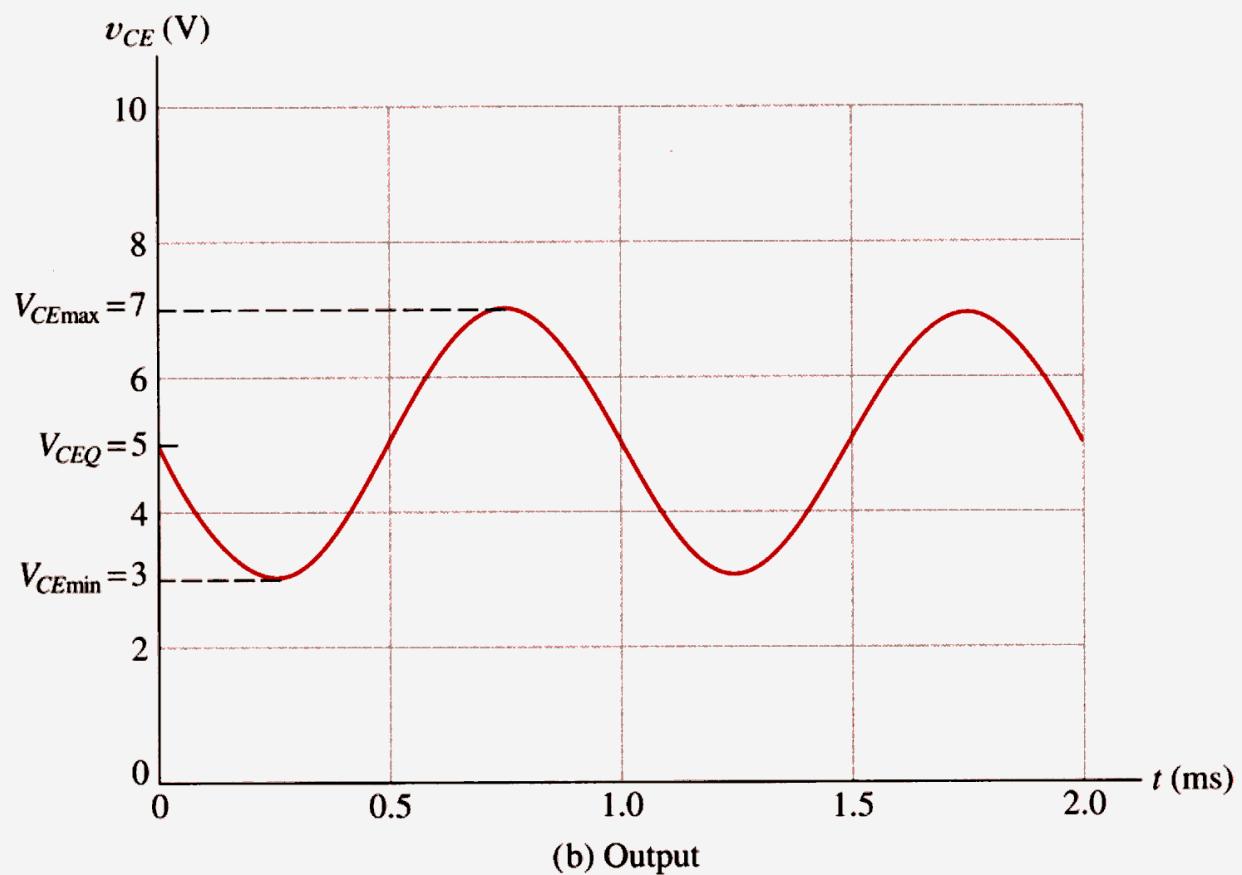
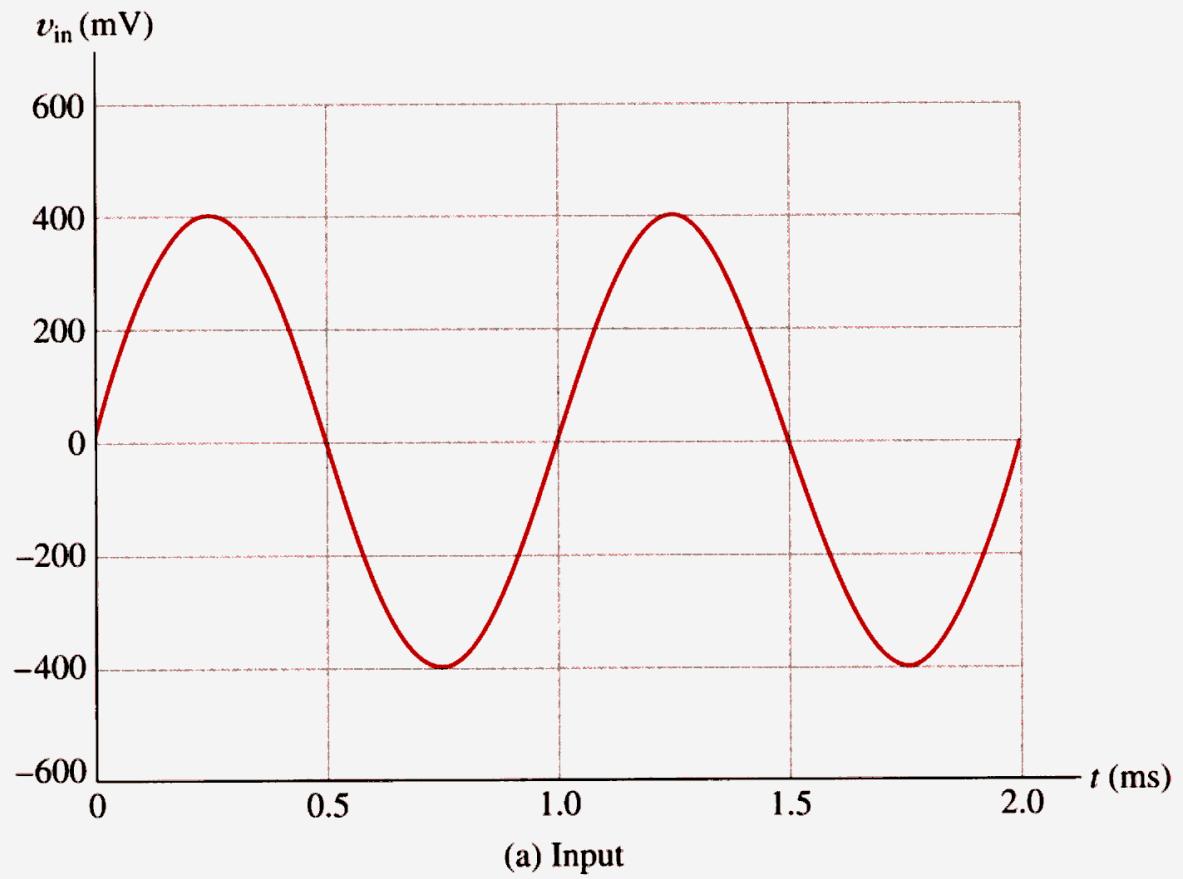


Figure 5.10 Voltage waveforms for the amplifier of Figure 5.7. See Example 5.2.


DISTORTION

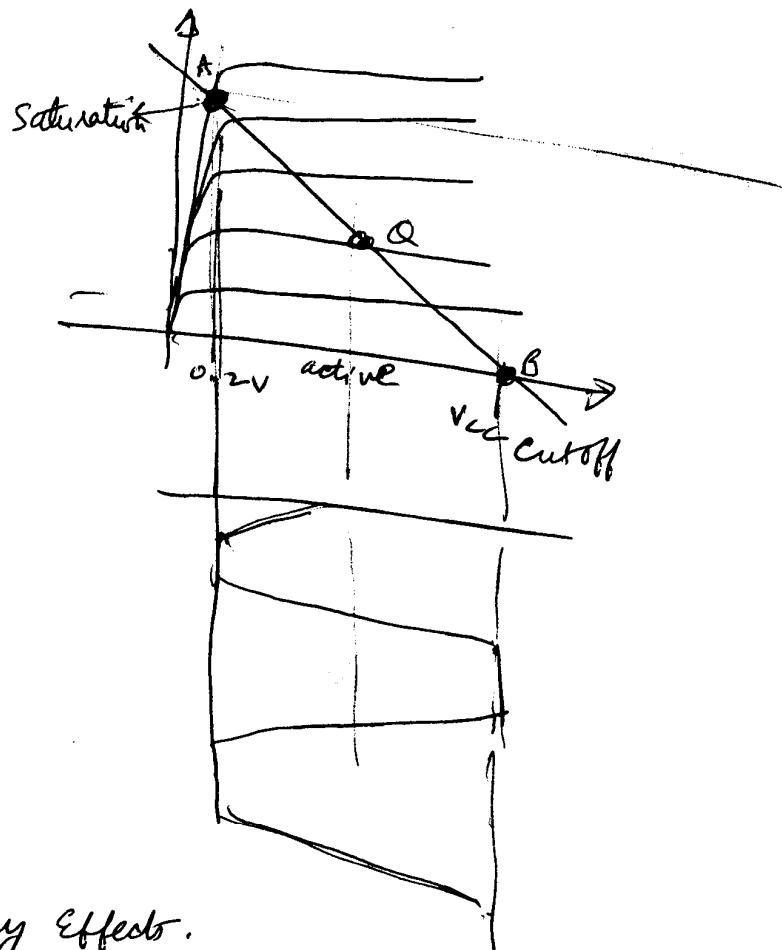
- The output is not a TRUE sinusoid depending on the input/output characteristics of the amplifier (transistor).



Secondary Effects:

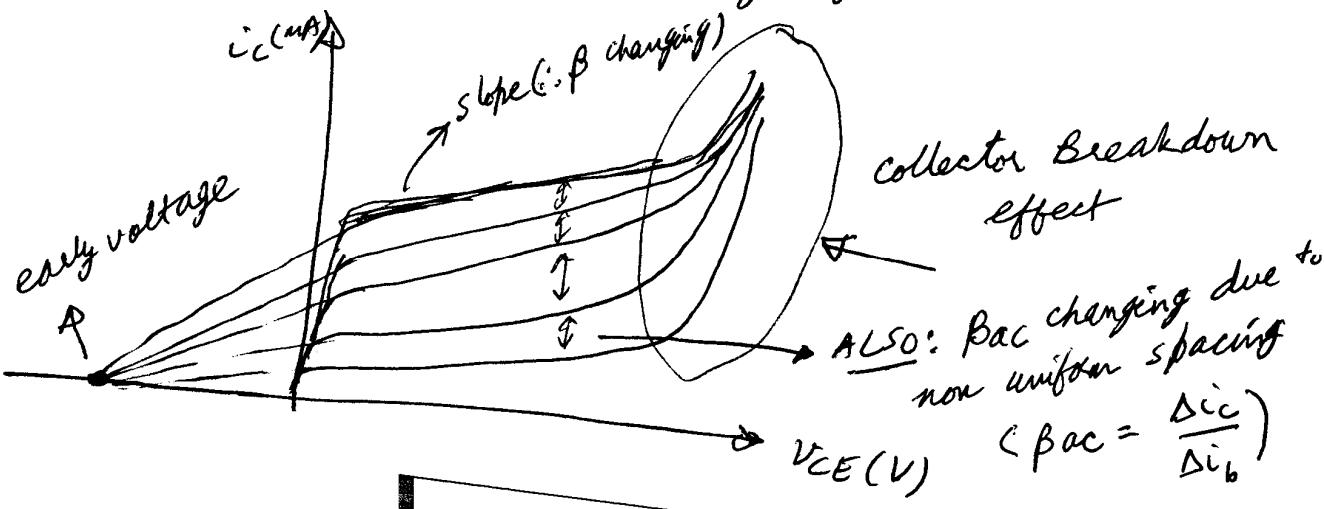Ideal model: First order model
Real BJTs show secondary effects.




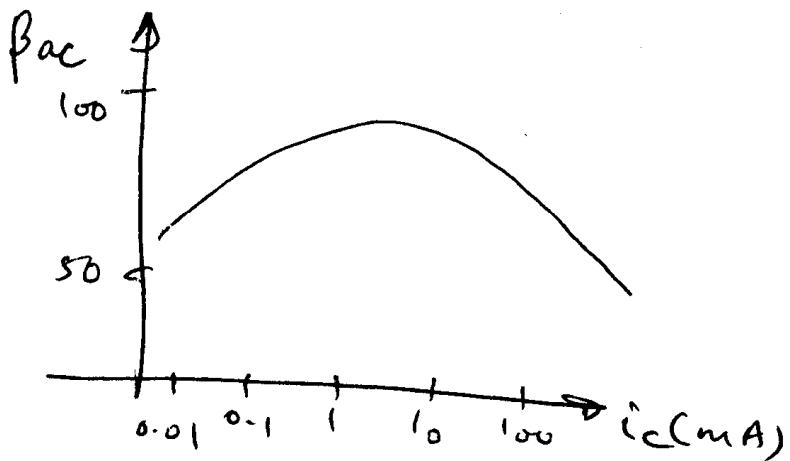

- β also varies from unit to unit.
- Typically ratio of highest value to lowest value of $\beta = 3:1$
- β also varies with temperature
- β and β_{ac} also vary with i_C

Since β and β_{ac} ~~also~~ vary, therefore many times β and β_{ac} used interchangeably; and also create designs which are insensitive to β variations.


Input characteristics secondary effect

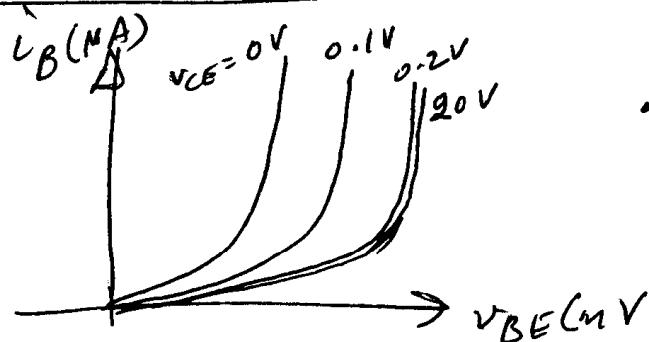



- Input curves change with V_{CB} .
- If $V_{CE} > 0.2V$ (here) then practically same curve.

High Frequency (Charge Storage Effects)

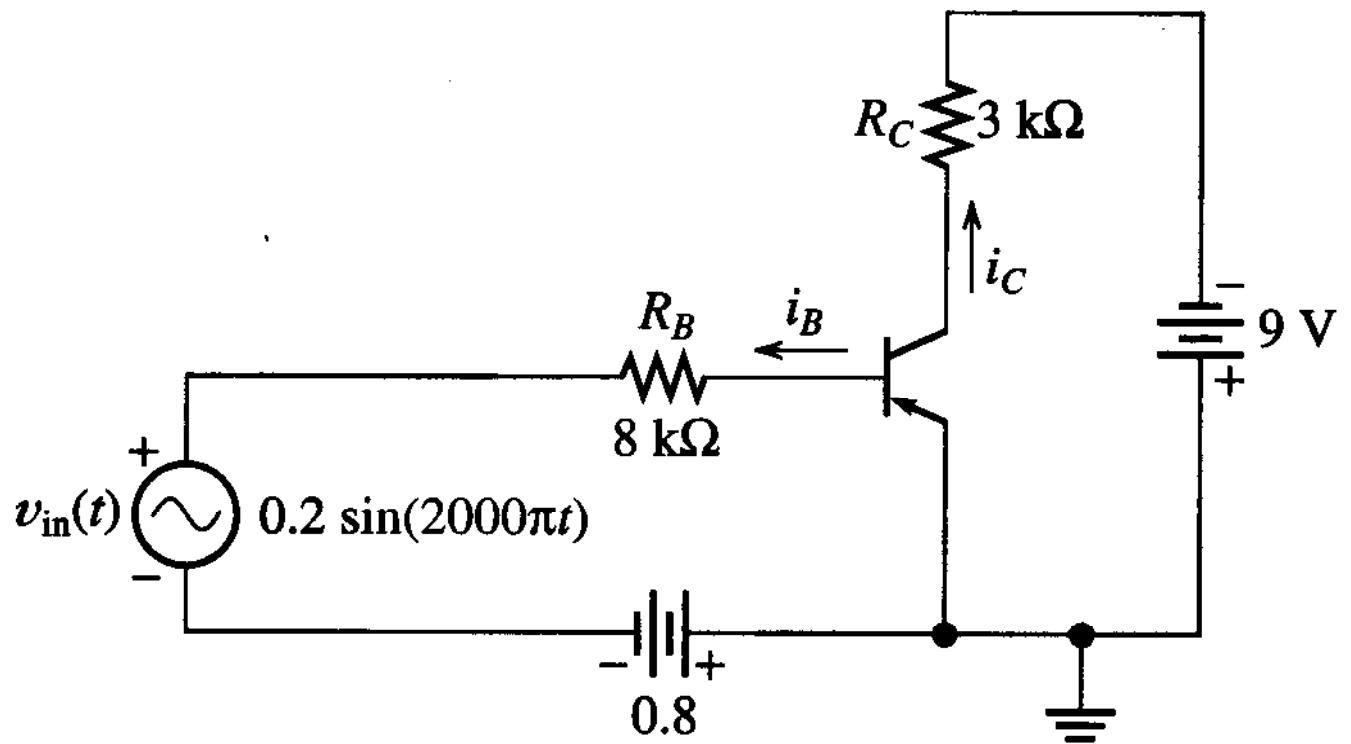
At high frequency we add capacitors in the BJT model (e.g. between B and C, and B and E etc.).




Common-emitter amplifier using PNP

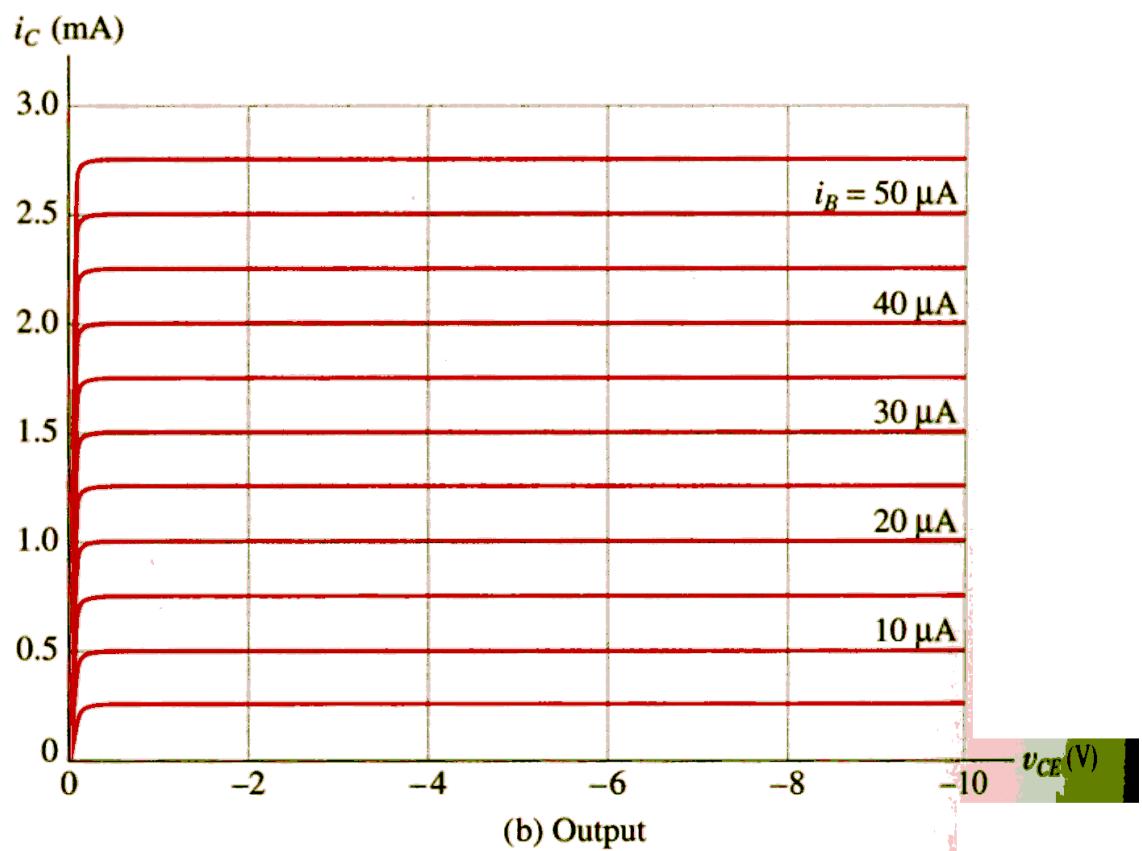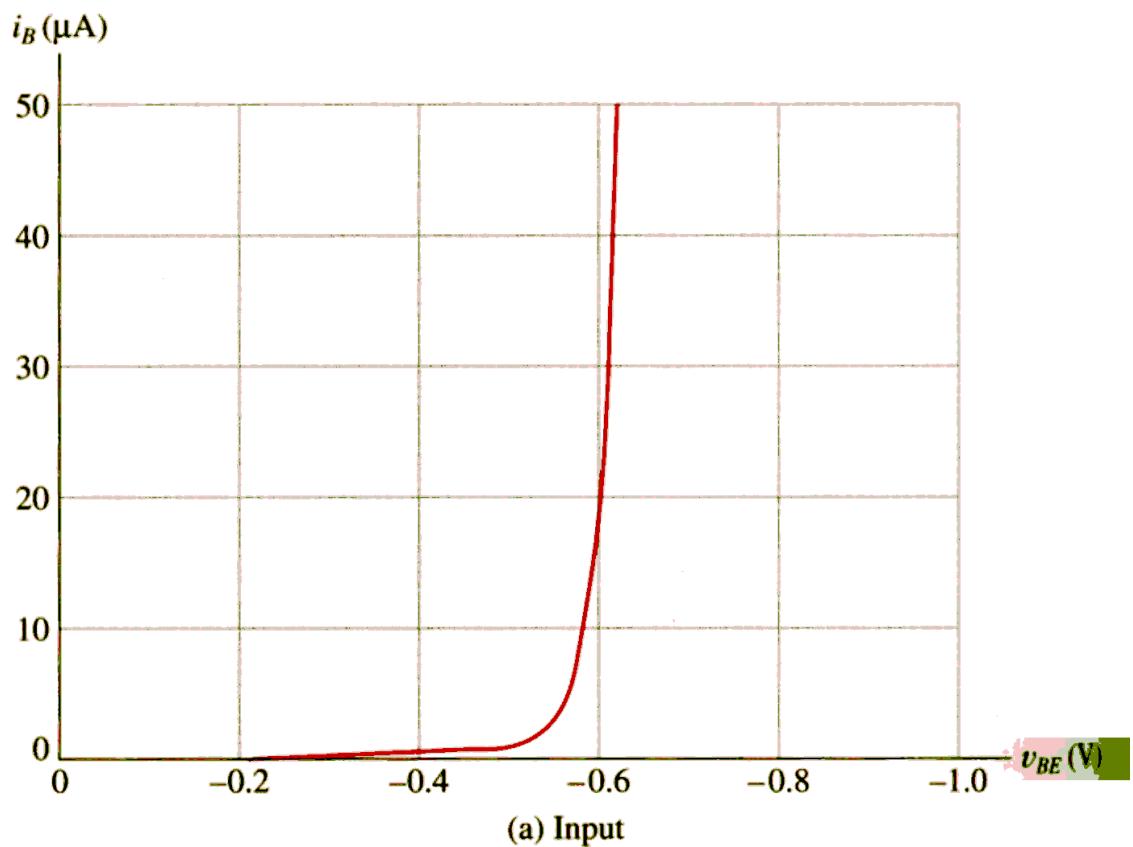

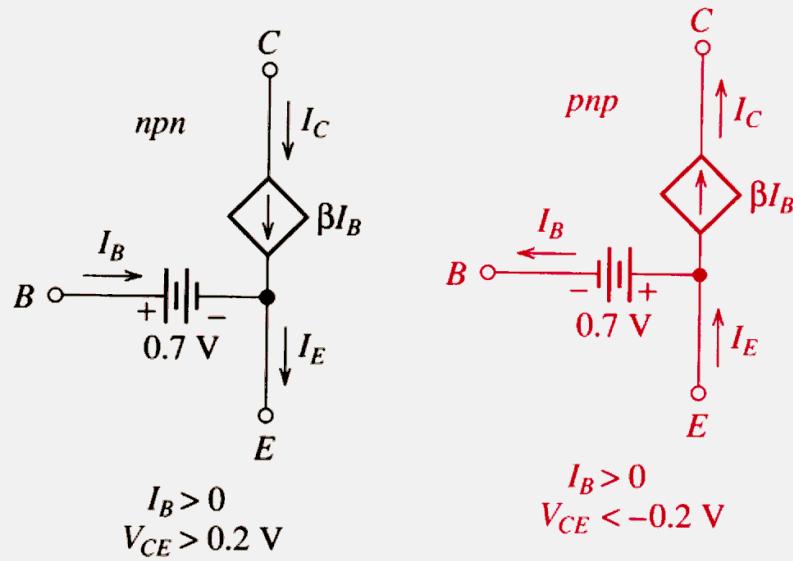
Common-emitter characteristics for a *pnp* BJT.



(a) Active region

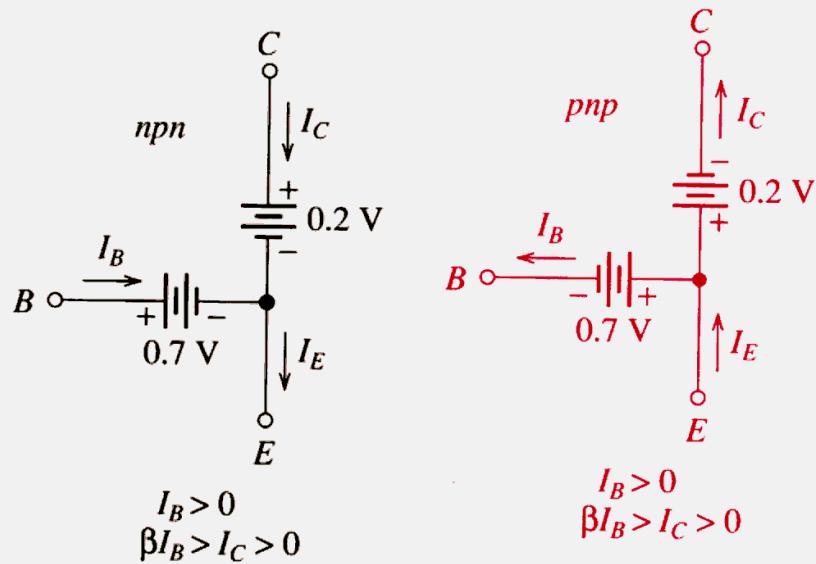


(b) Saturation region

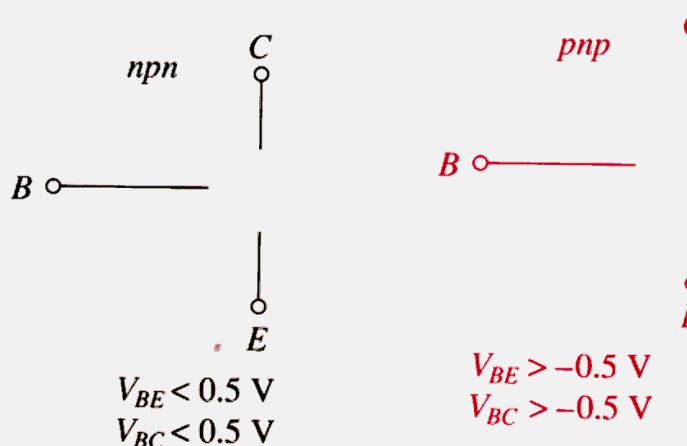


(c) Cutoff region

Figure 5.20
BJT large-signal models. (Note: Values shown are appropriate for typical small-signal silicon devices at a temperature of 300 K.)

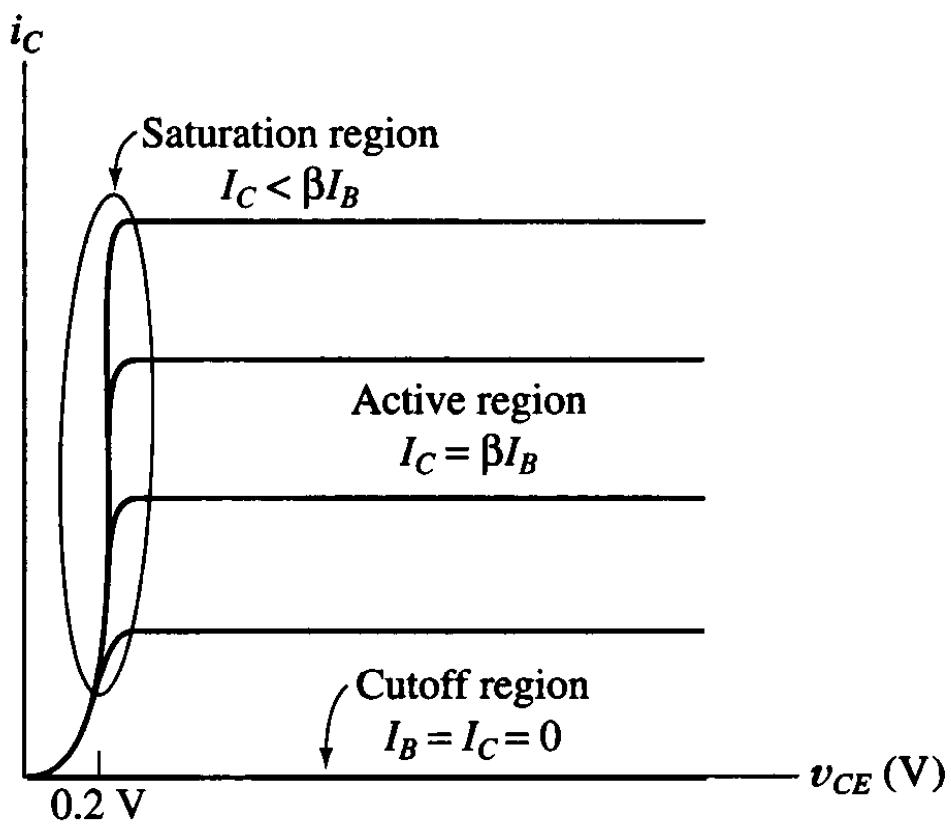


(a) Output characteristic

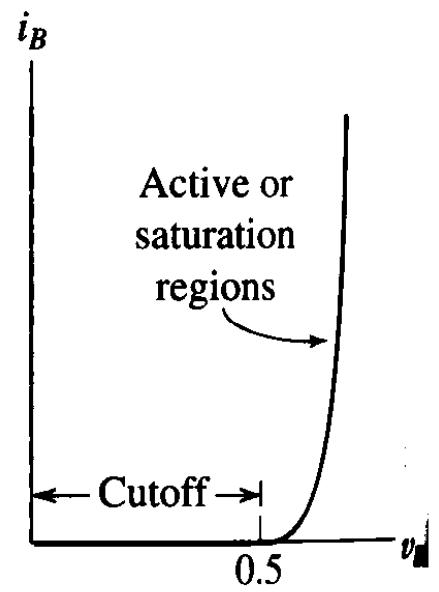

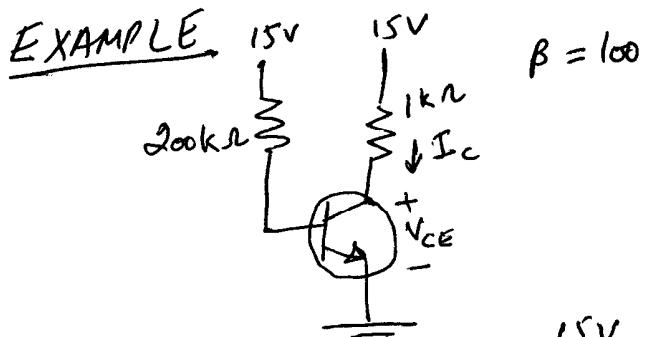
(b) Input characteristic

Large Signal DC Analysis.

just like diode analysis assume a region of operation and then check for consistency.



Assume: cut off:

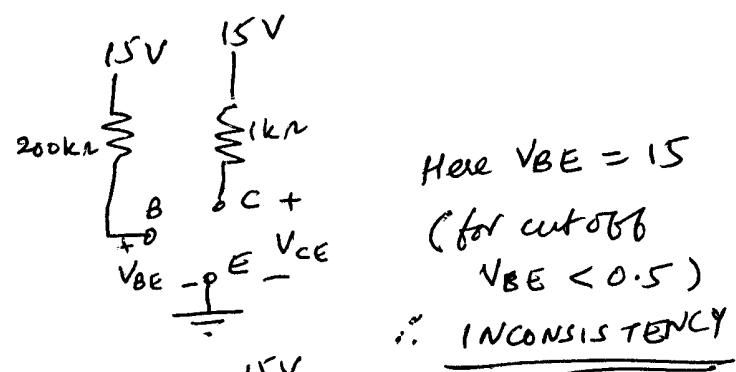


$$\text{Here } V_{BE} = 15$$

(for cut off
 $V_{BE} < 0.5$)

∴ INCONSISTENCY

Saturation:

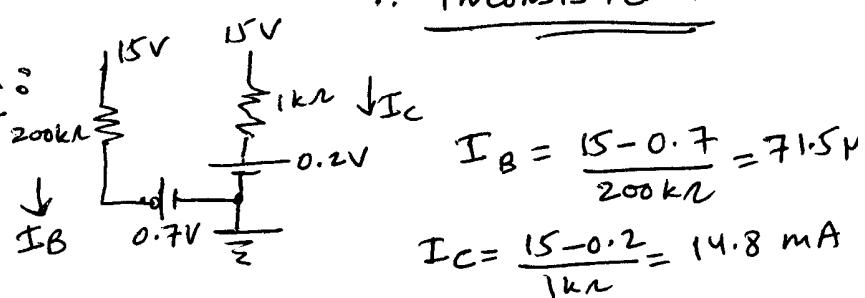

$$I_B = \frac{15 - 0.7}{200k\Omega} = 7.15 \mu\text{A}$$


$$I_C = \frac{15 - 0.2}{1k\Omega} = 14.8 \text{ mA}$$

Here $\beta I_B < I_C$

(should be $>$ for saturation)

inconsistent also

Active:

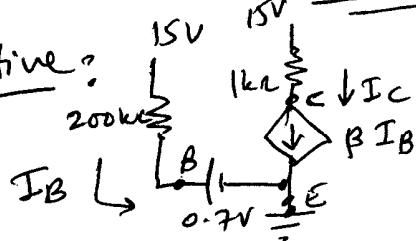

$$I_B = \frac{15 - 0.7}{200k\Omega} = 7.15 \mu\text{A}$$

$$I_C = \beta I_B = 7.15 \text{ mA}$$

$$V_{CE} = 15 - I_C(1k\Omega)$$


$$= 7.85 \text{ V}$$

$\therefore V_{CE} > 0.2 \text{ V}$ and $I_B > 0$

Transistor operate in ACTIVE region





BASE BIAS



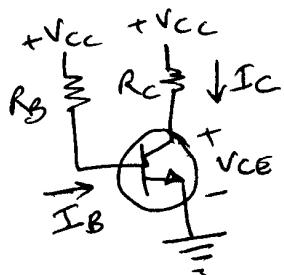


- I_B is controlled by V_{CC} and R_B
- α point sensitive to changes in β

EXAMPLE 5.4 + 5.5

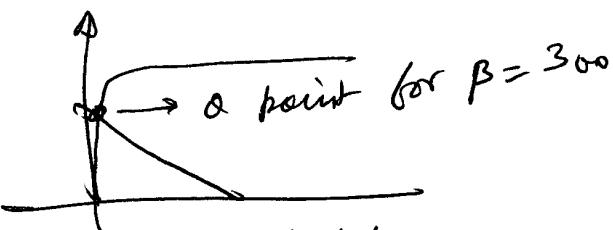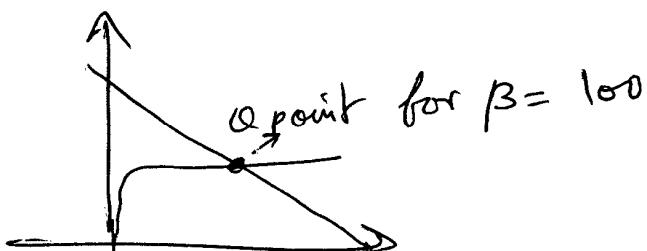


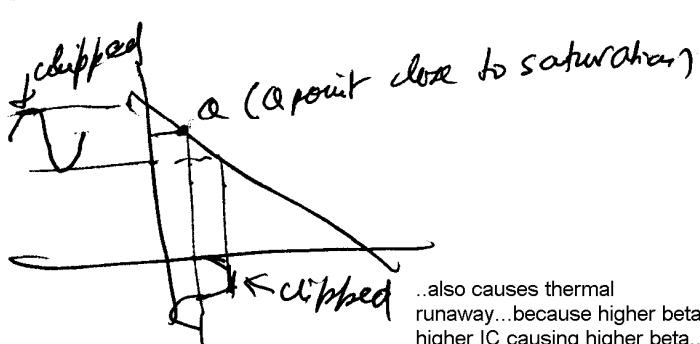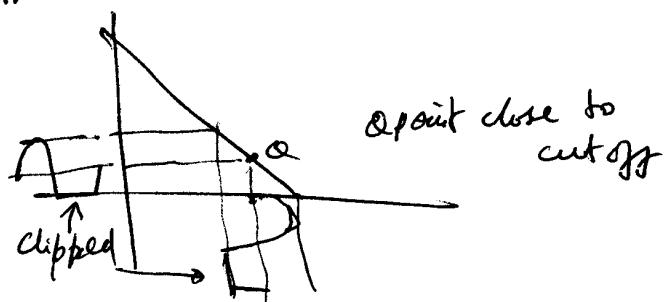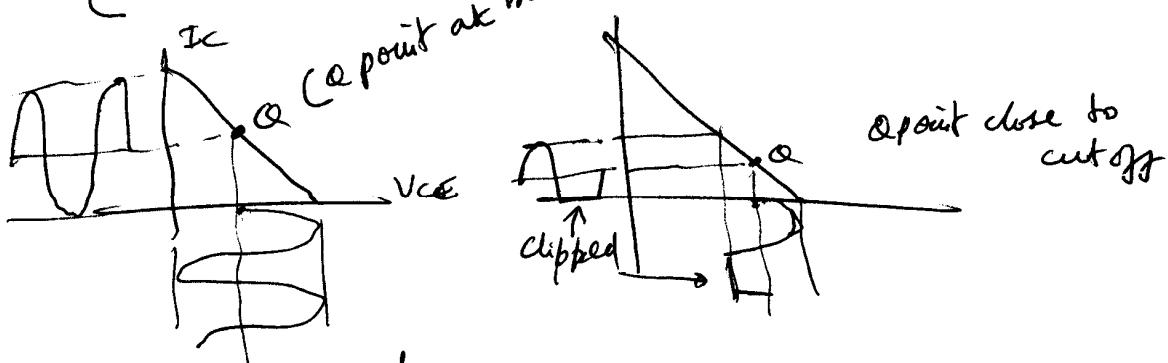- 1:3 variation is expected.
- Using this circuit, R_B would have to be adjusted to get Q in the middle (not practical)
- We need Q in the middle so that the AC signal can be amplified without distortion
(CLASS A amplifiers)




..also causes thermal runaway...because higher β causes higher I_C causing higher β ...

EMITTER BIAS

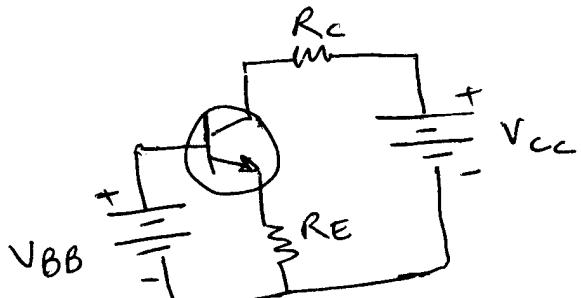

(A)

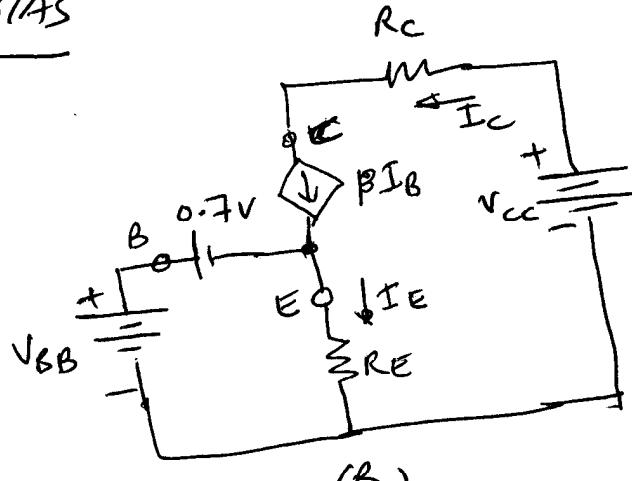

(B)

Assuming active region, we get (B) from (A)

$$V_{BB} = 0.7 + I_E R_E$$

$$\therefore I_E = \frac{V_{BB} - 0.7}{R_E} \quad (\text{Independent of } \beta)$$

$$I_C = \beta I_B \quad \text{and} \quad I_E = I_B + I_C$$

$$\therefore I_E = (\beta + 1) I_B$$

$$\therefore I_B = \frac{I_E}{\beta + 1}$$

$$\therefore I_C = \frac{\beta I_B}{(\beta + 1)} \quad (\text{Fairly constant for high } \beta)$$




$$V_{CC} = R_C I_C + V_{CE} + R_E I_E$$

$$V_{CE} = V_{CC} - R_C I_C - R_E I_E \quad (\text{Fairly constant again because of } I_C)$$

NOT VERY PRACTICAL STILL


- Two sources required (V_{BB} and V_{CC})
- For AC signals the base is at ground (\therefore doesn't allow AC signals to be fed at base).

VOLTAGE DIVIDER BIAS

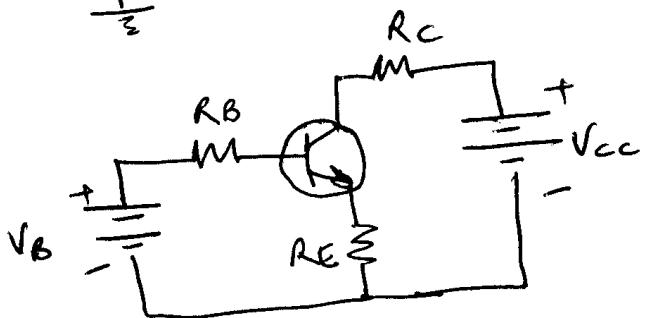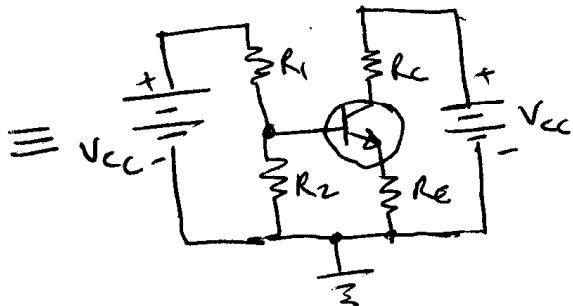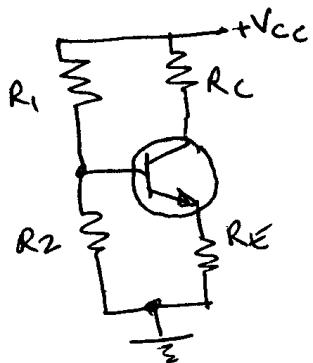

$$V_b = \frac{R_2 V_{cc}}{R_1 + R_2}$$
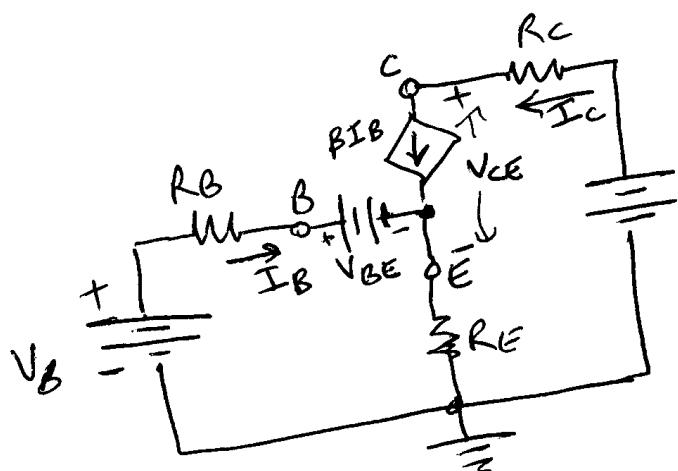
$$R_B = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = R_1 \parallel R_2$$



Usually $V_{BE} = 0.7 \text{ V}$

$$V_b = R_B I_B + V_{BE} + R_E I_E \quad \text{--- (1)}$$

$$\therefore I_E = (\beta + 1) I_B \quad \text{--- (2)}$$

$$\text{From (1) + (2)} \quad \therefore I_B = \frac{V_b - V_{BE}}{R_B + (\beta + 1) R_E} \quad \text{--- (3)}$$

$$V_{CE} = V_{cc} - R_C I_C - R_E I_E \quad \text{--- (4)}$$

$$\text{where } I_C = \beta I_B \text{ and } I_E = (\beta + 1) I_B \quad \text{--- (5)}$$

use (3) in (4) using (5)

to solve for V_{CE} .

DESIGN CONSIDERATIONS FOR VOLTAGE DIVIDER BIAS

Recall

$$I_B = \frac{V_B - V_{BE}}{R_B + (\beta + 1)R_E}$$

$$\text{and } I_C = \beta I_B \quad \text{and } I_E = (\beta + 1)I_B$$

\therefore If β is large and R_B is small

then $I_C = \beta I_B = \frac{\beta(V_B - V_{BE})}{(R_B + (\beta + 1)R_E)}$

$$\approx \frac{V_B - V_{BE}}{R_E} \quad (\text{independent of } \beta)$$

same for $I_E \dots$

$$\therefore V_{CE} = V_{CC} - R_C I_C - R_E I_E \quad (\text{sensitive to } \beta \text{ variations})$$

If R_B large, then I_C & V_{CE} vary with β .

so, keep R_1 and R_2 ~~large~~ small.

However, low R_1 and $R_2 \Rightarrow$ larger currents,
overheating & need for larger
(expensive) power supply.

\therefore Compromise values of R_1 and R_2

- choose R_2 so that current through $R_2 = 10$ (or 20 times)
largest I_B expected.

- $\therefore I_B = \frac{V_B - V_{BE}}{R_B + (\beta + 1)R_E}$ and V_{BE} varies with temperature,
make V_B larger than variations

- $V_B = \frac{1}{3}V_{CC}$; $V_{(across R_C)} = \frac{1}{3}V_{CC} = V_{(across R_E)}$
 $= V_{CE}$

- Use frequency response, peak signal swing,
availability, cost etc. constraints also.


TRANSISTOR MAXIMUM RATINGS

Maximum ratings are

V_{EB} , V_{CB} , V_{CE} voltages

$I_C(\max)$, $P_D(\max)$ (Power)

$T_j(\max)$ junction temperature

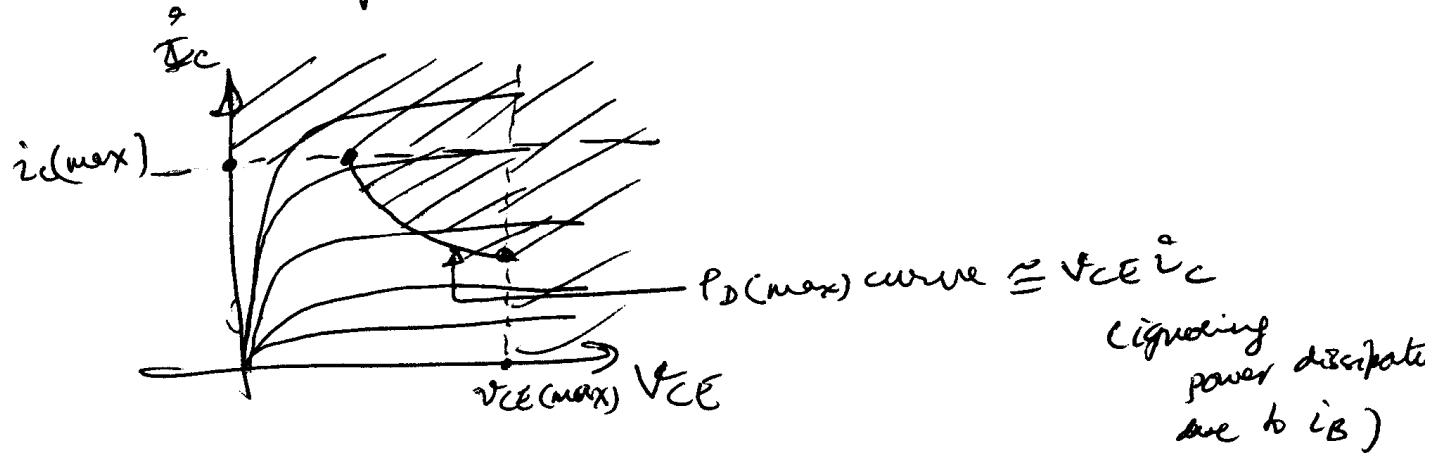


$$T_j = T_A + \theta_{JA} P_D$$

↓
junction temperature ↑ ambient temperature
↑ power dissipation

∴ θ_{JA} decreases with temperature.

Bias & Signal

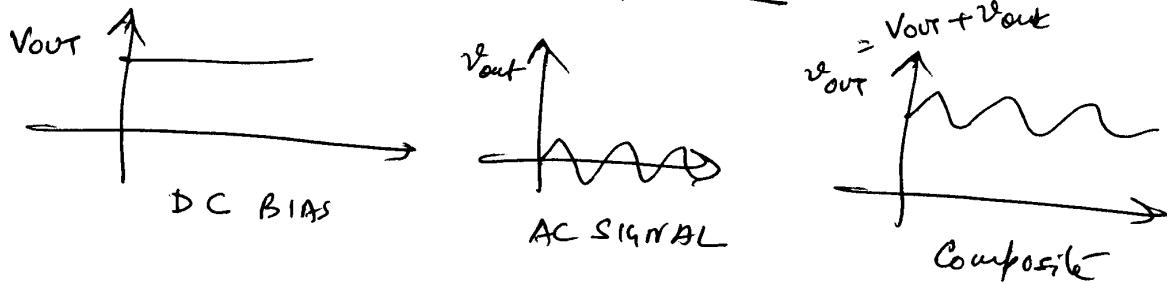

$$i_B(t) = I_{BQ} + i_b(t)$$

$$v_{BE}(t) = V_{BEQ} + v_{be}(t)$$


$$i_B = (1-\alpha) I_{ES} \left[\exp\left(\frac{v_{BE}}{V_T}\right) - 1 \right]$$

$$I_{BQ} + i_b(t) = (1-\alpha) I_{ES} \exp\left[\frac{V_{BEQ} + v_{be}(t)}{V_T}\right] \quad \text{in active region}$$

$$= (1-\alpha) I_{ES} \exp\left(\frac{V_{BEQ}}{V_T}\right) \exp\left(\frac{v_{be}(t)}{V_T}\right)$$

"1" is ignored

ALTERNATE DERIVATION

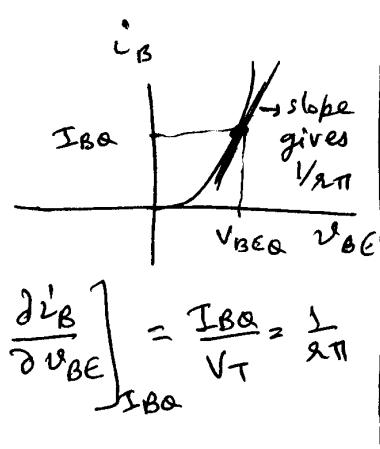

$$\left[\frac{di_B}{dv_{BE}} \right]_{I_BQ} = \frac{I_{BQ}}{V_T} = \frac{1}{R_\pi}$$

$$\therefore I_{BQ} + i_b(t) = I_{BQ} \exp\left(\frac{v_{be}(t)}{V_T}\right)$$

Here v_{be} is very small, \therefore using for $|x| \ll 1$, $\exp(x) = 1+x$

$$I_{BQ} + i_b(t) \approx I_{BQ} \left(1 + \frac{v_{be}(t)}{V_T} \right)$$

$$i_b(t) = \frac{I_{BQ}}{V_T} v_{be}(t)$$

define $\frac{V_T}{I_{BQ}} = R_\pi$, then $i_b(t) = \frac{v_{be}(t)}{R_\pi}$

since $I_{BQ} = I_C Q / \beta \Rightarrow R_\pi = \frac{\beta V_T}{I_C Q}$

Typical value of $R_\pi = 2600 \Omega$

Total current $i_C(t) = \beta i_B(t)$


also $I_C Q = \beta I_{BQ}$

$$\therefore I_C Q + i_c(t) = \beta I_{BQ} + \beta i_b(t)$$


$$\therefore \boxed{i_c(t) = \beta i_b(t)}$$

Small Signal Model for BJT

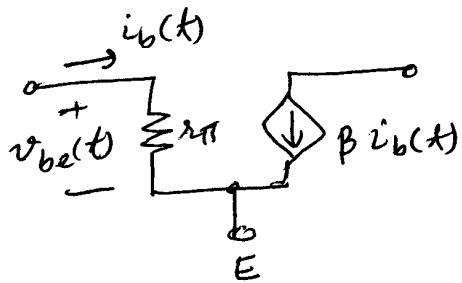- Small signal model is EXACTLY the same for NPN and PNP.




Coupling Capacitors.

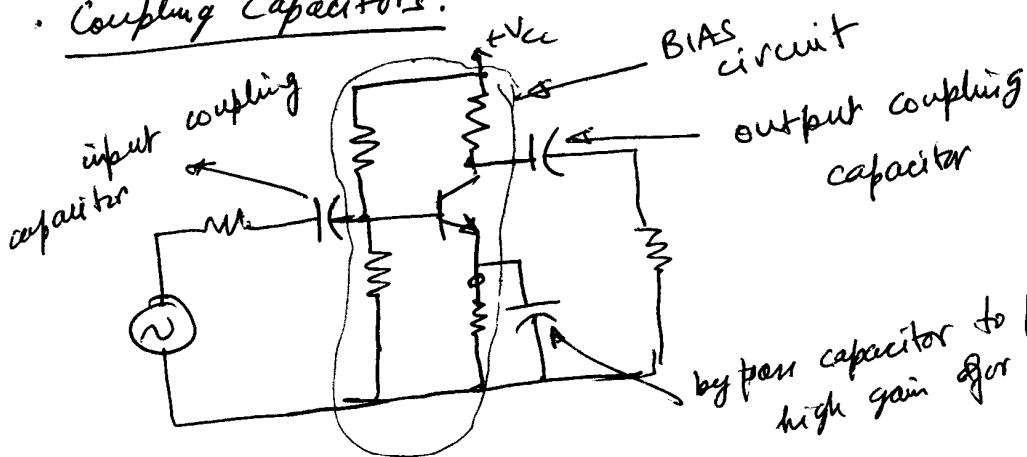

by pass capacitor to produce high gain for AC.

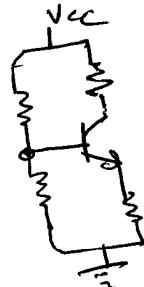For DC, capacitor is open,
 \therefore DC circuit is \rightarrow
 which gives us a point




For AC, capacitor is a short

(also all DC sources are grounded).

Capacitor Impedance = $\frac{1}{j\omega C} - \frac{1}{\omega C}$ ($= 0$ at high frequency
 but large (∞)

\therefore If the signal has very low frequency, then the capacitor is not a short, and at very high frequencies, the model for BJT is changed (additional capacitance added.)


For low impedance to AC

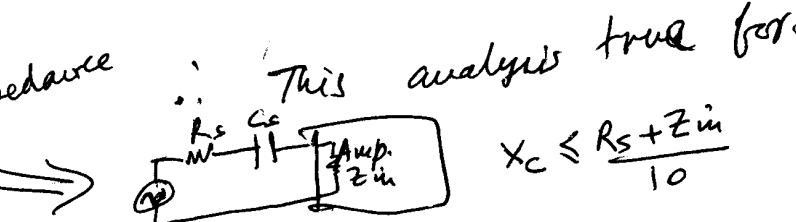


\therefore This analysis true for

$$X_C \leq \frac{R_S + Z_{in}}{10}$$


MID FREQUENCY RANGE

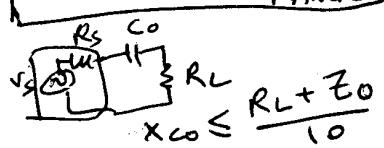


$$X_{C0} \leq \frac{R_L + Z_0}{10}$$

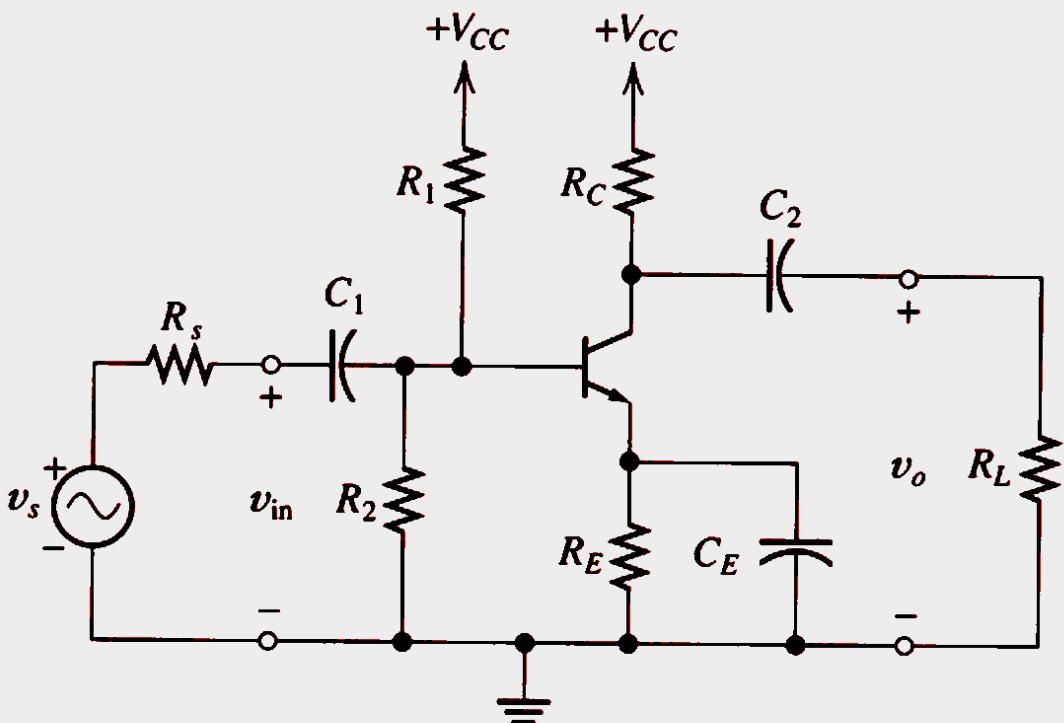

(a) Actual circuit

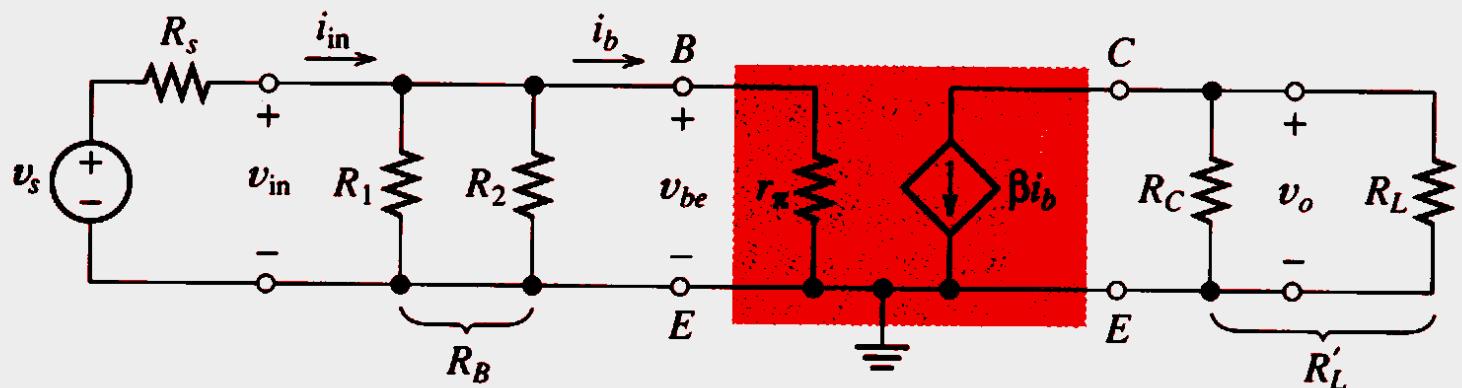

(b) Small-signal ac equivalent circuit

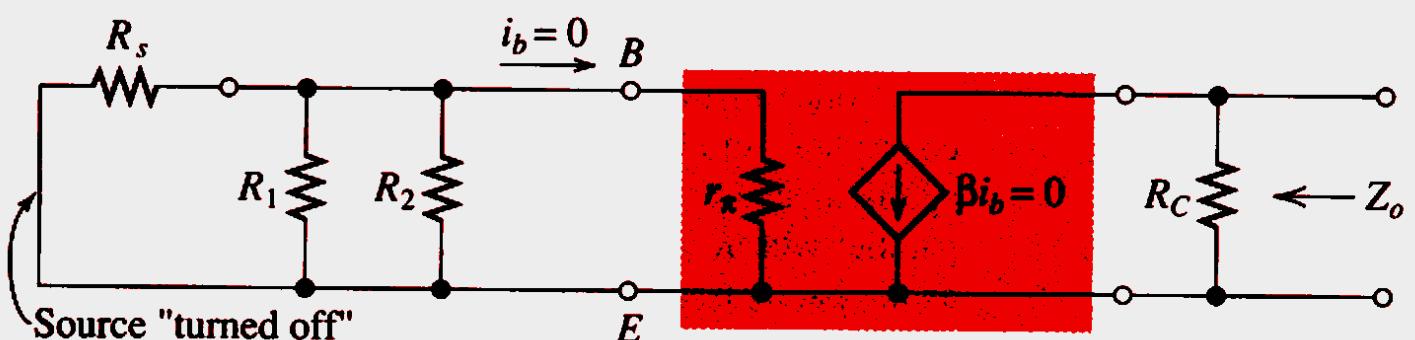

(c) Equivalent circuit used to find Z_o

Figure 5.32 Common-emitter amplifier.

Common Emitter Amplifier (Small Signals)

VOLTAGE GAIN

$$V_{in} = V_{be} = i_b R_{\pi}$$

$$V_o = -R_L \beta i_b$$

$$\therefore A_v = \frac{V_o}{V_{in}} = -\frac{\beta R_L}{R_{\pi}}$$

$$A_v = -\frac{\beta R_L}{R_{\pi}}$$

-ve sign to show inverting amplifier.

also $A_v^o = \frac{-\beta R_C}{R_{\pi}}$
 open circuit gain

LARGE VOLTAGE GAIN for common emitter.

INPUT IMPEDANCE

$$Z_{in} = \frac{V_{in}}{I_{in}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_{\pi}}}$$

CURRENT GAIN

$$A_i = \frac{i_o}{i_{in}} = \frac{A_v Z_{in}}{R_L}$$


Power Gain

$$G_p = A_L A_v$$


OUTPUT IMPEDANCE

set source voltage = 0 and then look at impedance from the output terminal.


$$Z_o = R_C$$

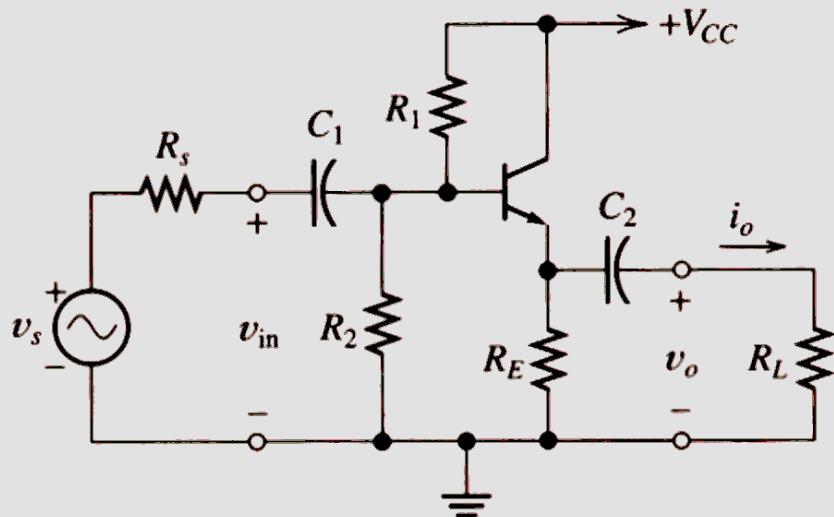

(a) Actual circuit

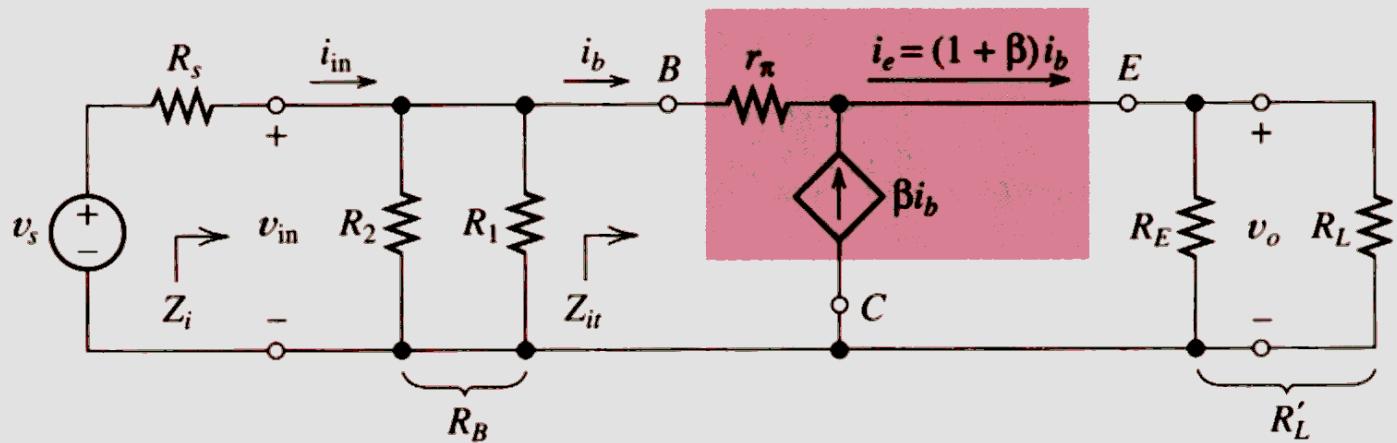

(b) Small-signal equivalent circuit

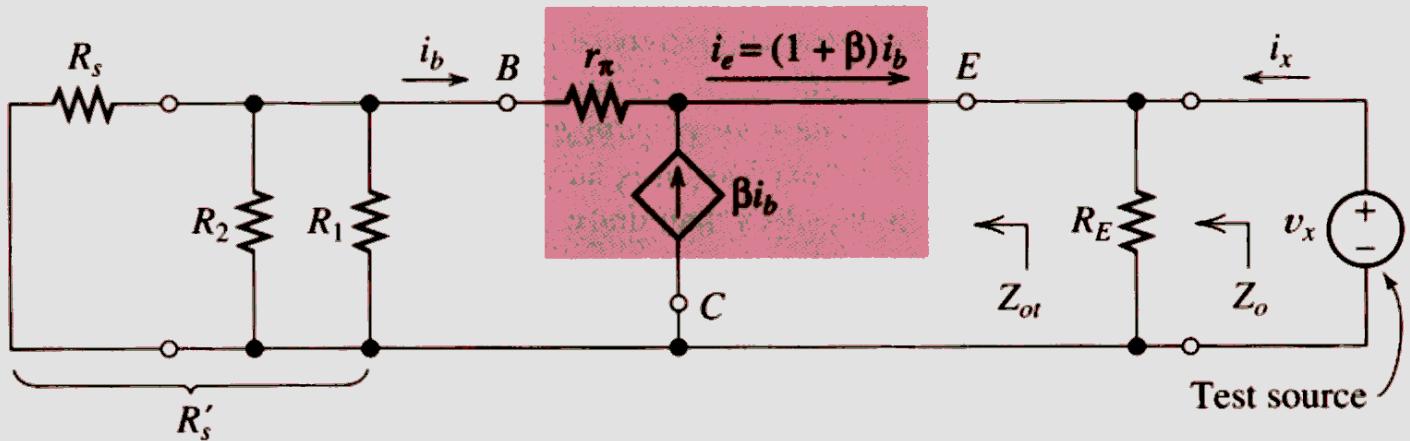

(c) Equivalent circuit used to find output impedance Z_o

Figure 5.35 Emitter follower.

EMITTER FOLLOWER (Small Signal)

VOLTAGE GAIN

$$v_o = R'_L (1+\beta) i_b \quad -\textcircled{1}$$

$$v_{in} = r_T i_b + (1+\beta) i_b R'_L \quad -\textcircled{2}$$

$$\therefore A_v = \frac{R'_L (1+\beta)}{r_T + (1+\beta) R'_L}$$

- (3) (notice $A_v < 1$) (close to 1)
 - non inverting (follower)
 - can provide current gain

INPUT IMPEDANCE

$$Z_i = \frac{1}{\frac{1}{R_1 + R_2} + \frac{1}{Z_{in}}}$$

$$Z_{in} = \frac{v_{in}}{i_b} \quad (\text{use } \textcircled{2}) = \boxed{r_T + (1+\beta) R'_L} \quad -\textcircled{4}$$

- Relatively high compared to other BJT configurations
- Can get higher using FETs and also using feedback

OUTPUT IMPEDANCE

- Remove load
- Turn off signal sources
- Look in from output terminals

$$Z_o = \frac{v_x}{i_x} \quad -\textcircled{5}$$

KCL at output node \Rightarrow

$$i_b + \beta i_b + i_x = \frac{v_x}{R_E} \quad -\textcircled{6}$$

$$\text{define } R'_S = \frac{1}{\frac{1}{R_S} + \frac{1}{R_1} + \frac{L}{R_2}} \quad -\textcircled{7}$$

$$\left. \begin{array}{l} \text{at KVL} \\ \text{at output} \\ \text{outside} \\ \text{loop all} \\ \text{the way} \end{array} \right\} v_x + r_T i_b + R'_S i_b = 0 \quad -\textcircled{8}$$


Replace i_b in $\textcircled{6}$ using $\textcircled{8}$ to get

$$Z_o = \frac{v_x}{i_x} = \frac{1}{\frac{(1+\beta)}{(R'_S + r_T)} + \frac{L}{R_E}} \quad -\textcircled{9}$$


which is $Z_o = R_E // Z_{out}$

$$\text{where } Z_{out} = \frac{R'_S + r_T}{(1+\beta)}$$

- Relatively low output impedance.

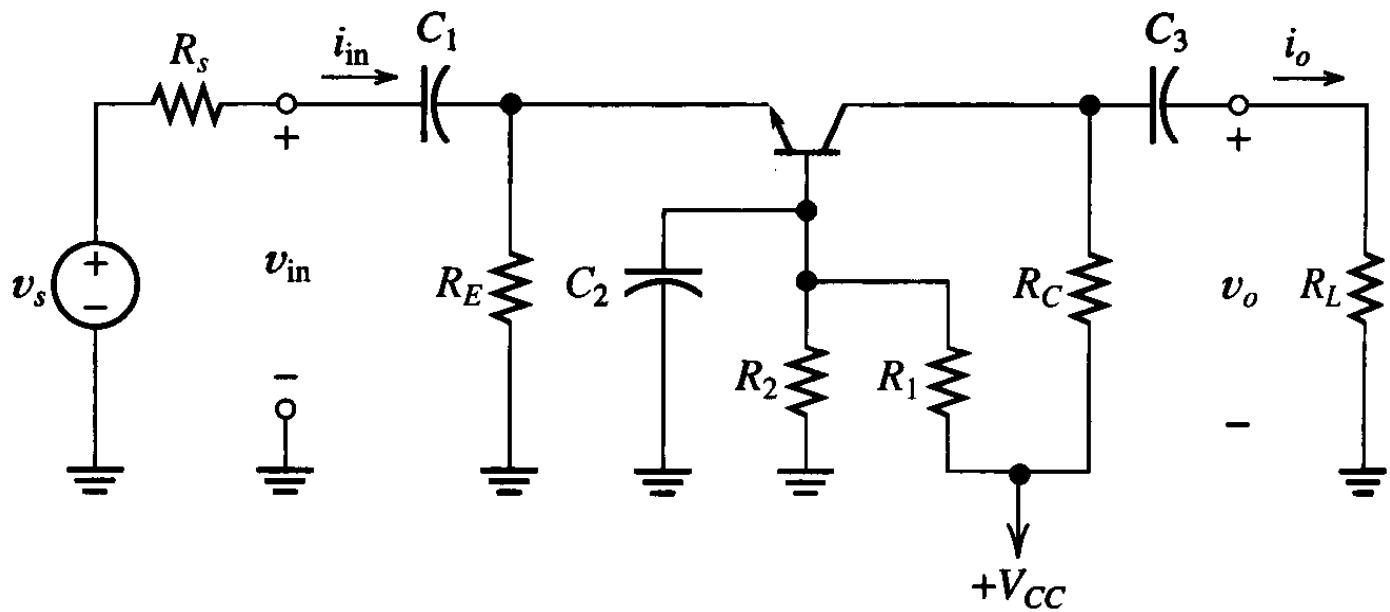

Common-base amplifier circuit.

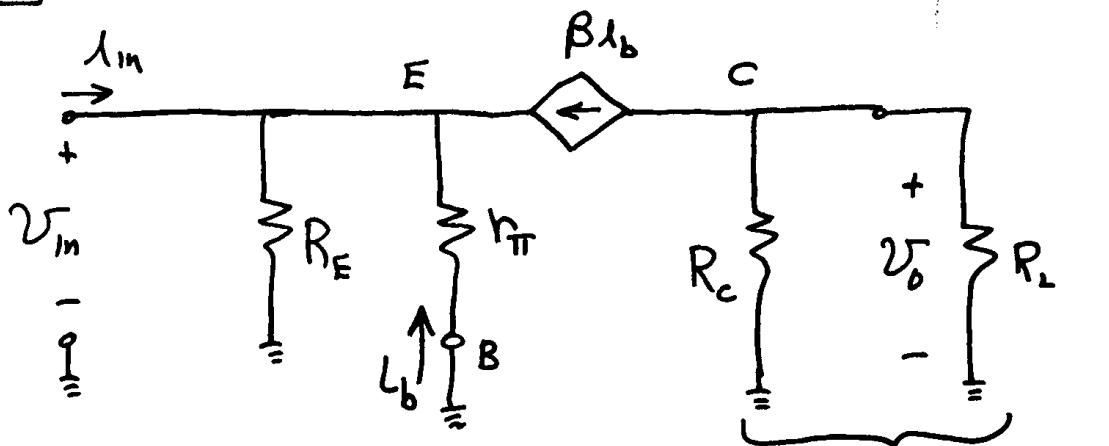

$$V_{in} = -r_{\pi} I_b$$

$$R'_L = \frac{1}{\frac{1}{R_C} + \frac{1}{R_L}}$$

$$V_o = -\beta I_b R'_L$$


$$A_v = \frac{V_o}{V_{in}} = \frac{\beta R'_L}{r_{\pi}}$$

$$I_{in} = \frac{V_{in}}{R_E} - (\beta + 1) I_b$$

$$I_{in} = \frac{V_{in}}{R_E} + \frac{\beta + 1}{r_{\pi}} V_{in}$$

$$R_{in} = \frac{V_{in}}{I_{in}} = \frac{1}{\frac{1}{R_E} + \frac{\beta + 1}{r_{\pi}}}$$

Output resistance:

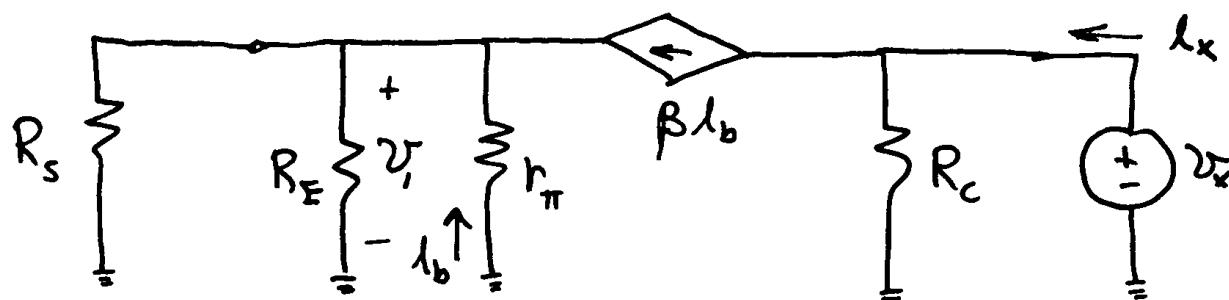

$$\left. \begin{aligned} \frac{V_i}{R_s} + \frac{V_i}{R_E} &= I_b + \beta I_b \\ V_i &= -r_{\pi} I_b \end{aligned} \right\} \Rightarrow I_b + \beta I_b + \frac{r_{\pi}}{R_s} I_b + \frac{r_{\pi}}{R_E} I_b = 0$$


$$\therefore I_b = 0$$

$$R_o = \frac{V_x}{I_x} = R_C$$

SUMMARY (section 5.12)

• Drawing Small Signal Equivalent Circuit

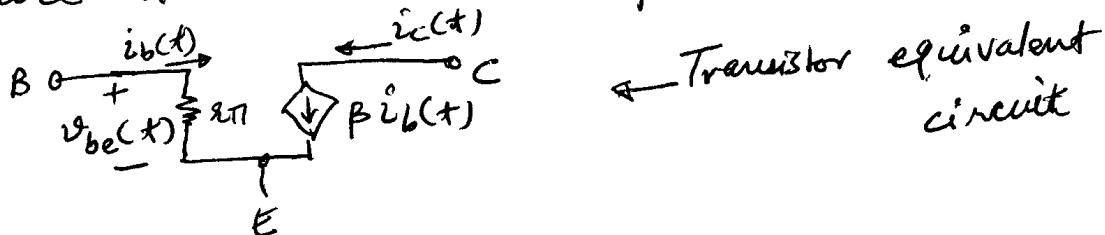- ① Replace dc voltage supply by a short.
- ② " " current " " open circuit.
- ③ For mid frequency analysis, replace capacitors by shorts.
- ④ Replace inductors by open circuit.
- ⑤ Replace transistor with its equivalent circuit.



• Identify circuit variables of interest

• Finding output impedance

- ① Turn off independent sources (voltage & current; make them zero)


② Remove the load

- ③ Find impedance looking in from output terminals
(might have to feed in test voltage V_x and then divide that by E_x)


• Write circuit equations

• Find and check the derived expression


• Check units.

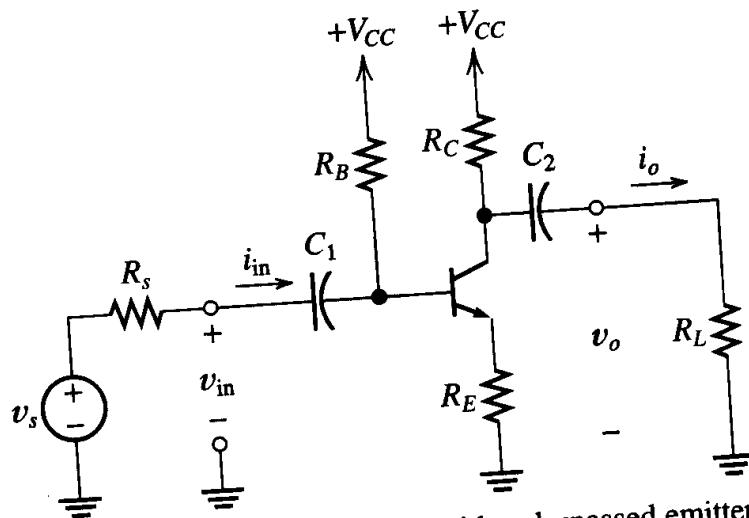

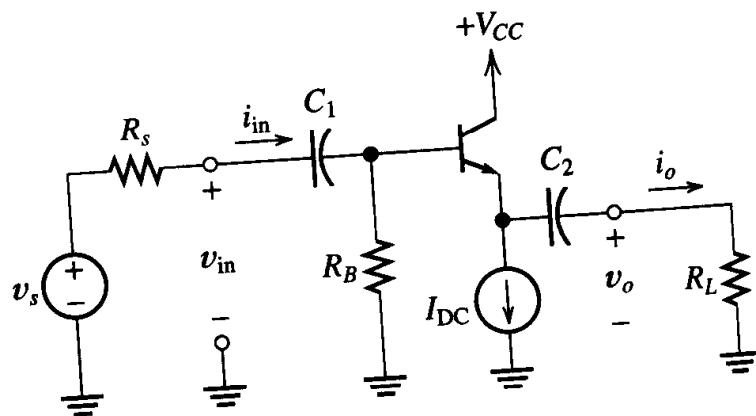(a) Common-emitter amplifier with unbypassed emitter resistor




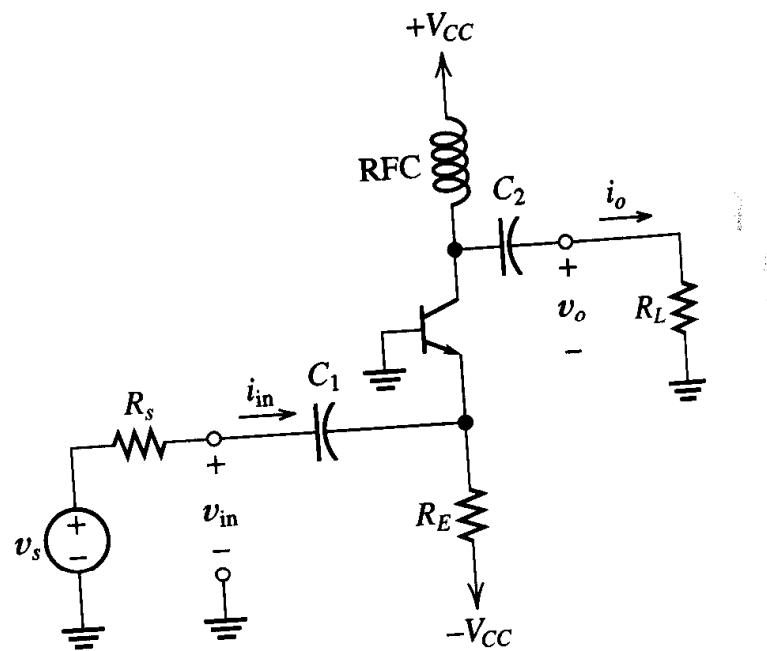(b) Variation of the emitter follower using a dc current source for biasing




(c) Variation of the common-base amplifier [assume that the *radio-frequency choke* (RFC) is an open circuit for the ac signals]


Figure 5.40 Amplifier circuits.

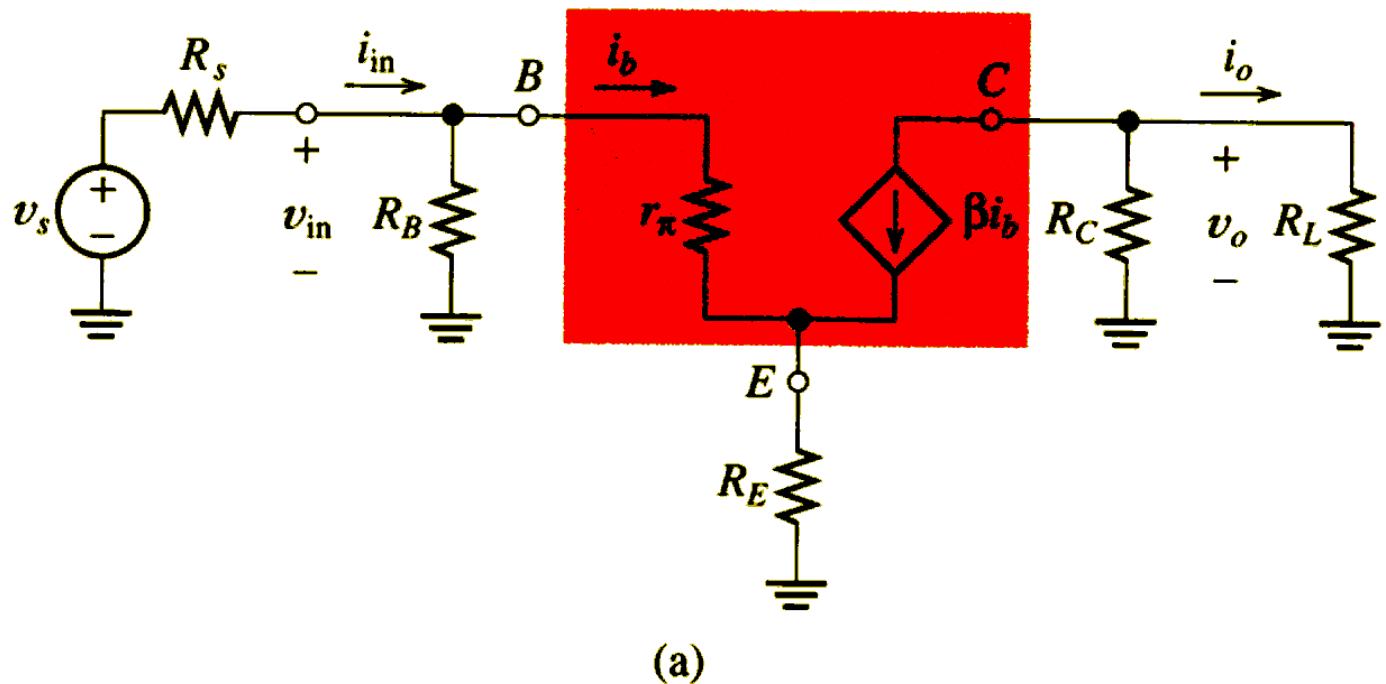

(a)

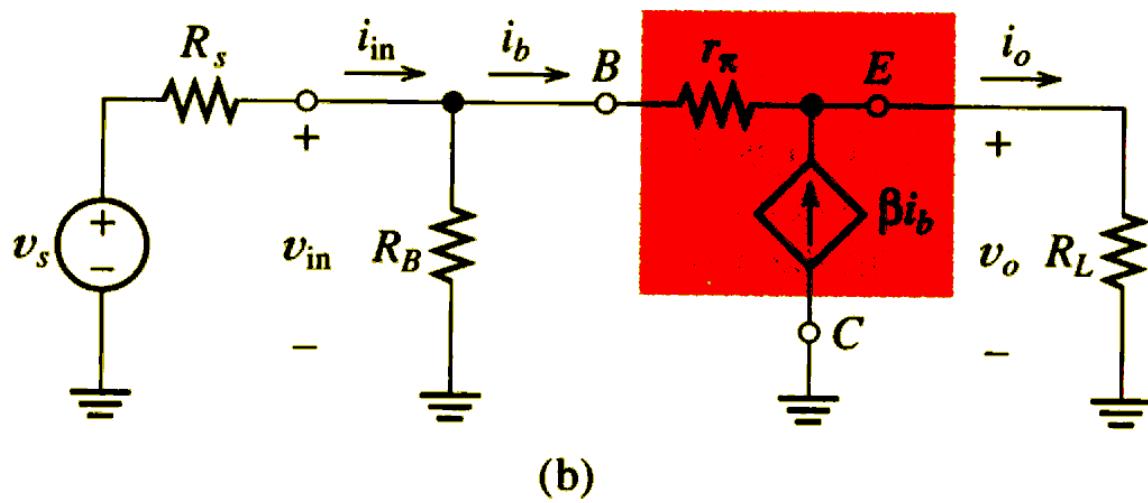




(b)

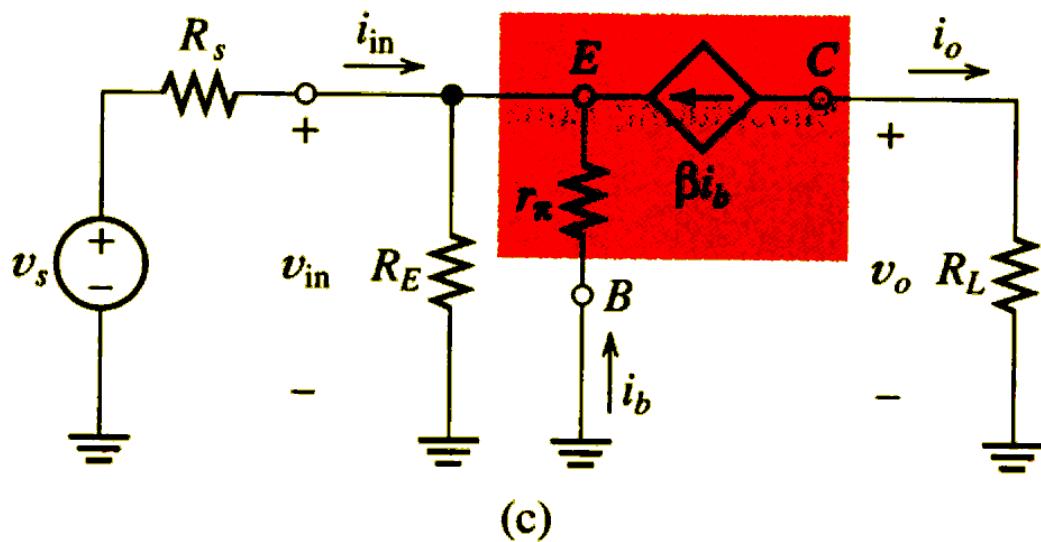


(c)


Figure 5.41 Small-signal equivalent circuits for the circuits of Figure 5.40.

Summary of Amplifier Configurations

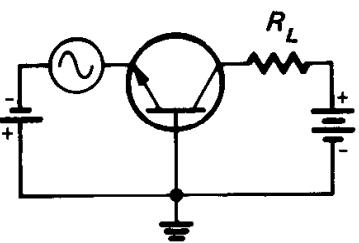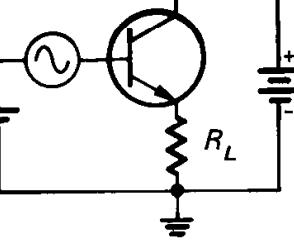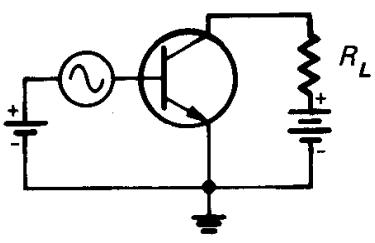	Common Base	Common Collector	Common Emitter
Basic circuit (Showing signal source and load R_L)			
Power gain	Yes	Yes	Yes (highest)
Voltage gain	Yes	No (less than 1)	Yes
Current gain	No (less than 1)	Yes	Yes
Input impedance	Lowest ($\approx 50 \Omega$)	Highest ($\approx 300 \text{ k}\Omega$)	Medium ($\approx 1 \text{ k}\Omega$)
Output impedance	Highest ($\approx 1 \text{ M}\Omega$)	Lowest ($\approx 300 \Omega$)	Medium ($\approx 50 \text{ k}\Omega$)
Phase inversion	No	No	Yes
Application	Used mainly as an RF amplifier	Used mainly as an isolation amplifier	Universal—works best in most applications

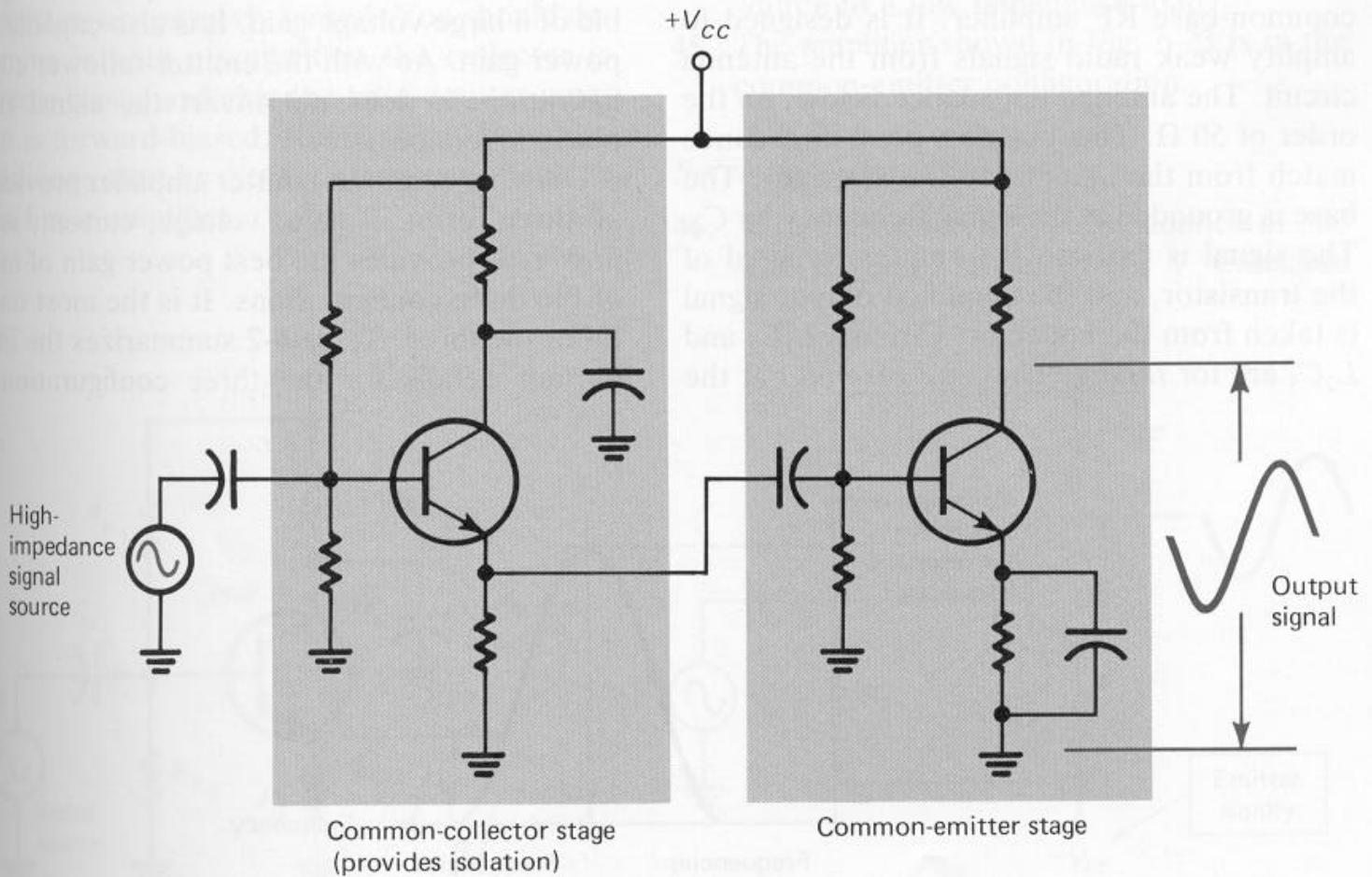

BJT as a switch (or an Inverter)

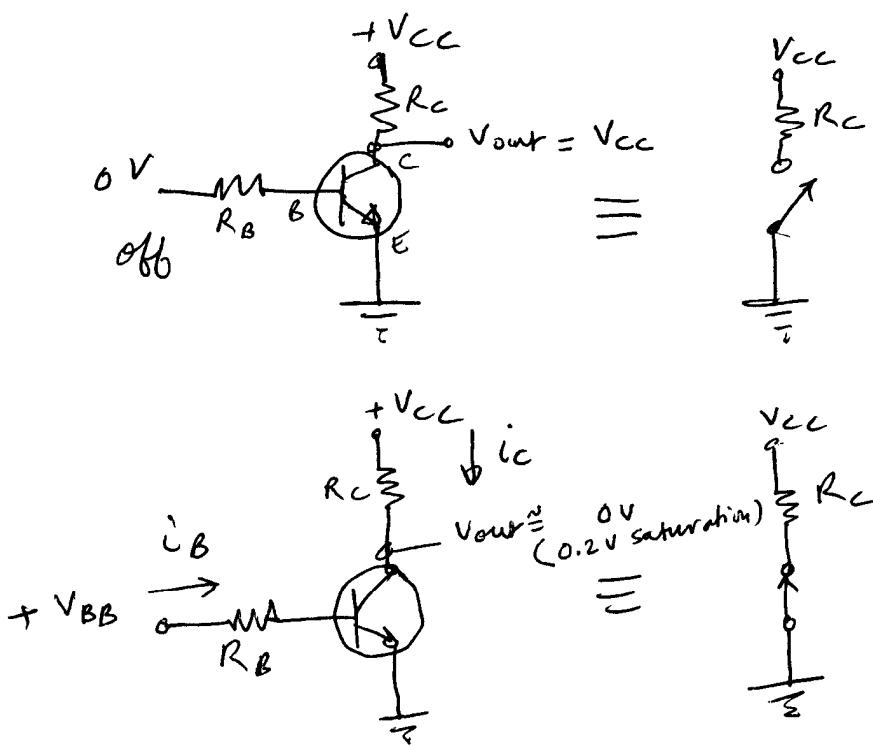

$$V_{out} = (V_{in})' \quad (V_{out} = \text{complement of } V_{in})$$

Condition in cutoff: $V_{CE} = V_{CC}$


Condition in Saturation:


$$i_C = \frac{V_{CC} - 0.2}{R_C} \quad (\text{sometimes used as } \frac{V_{CC}}{R_C})$$

Minimum Value of i_B needed for saturation: $\frac{i_C(\text{sat})}{\beta}$

Equation to calculate i_B (using input characteristic as is)

$$V_{BB} = i_B R_B + 0.7$$

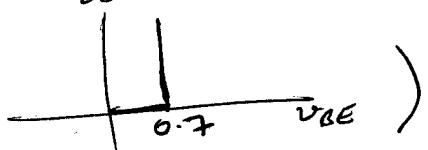

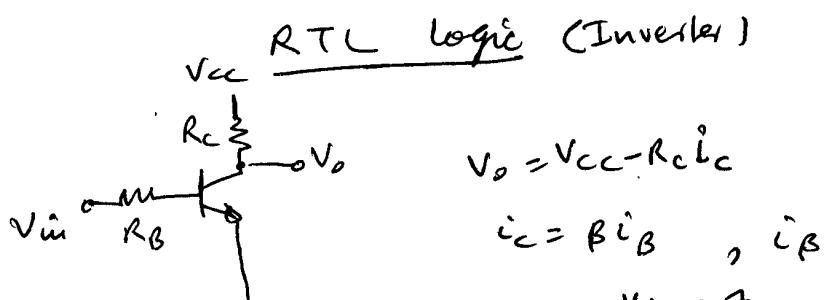

$$V_o = V_{CC} - R_c i_C$$

$$i_C = \beta i_B, \quad i_B = \frac{V_{IN} - 0.7}{R_B}$$

$$\therefore i_C = \beta \frac{V_{IN} - 0.7}{R_B}$$

$$V_o = V_{CC} - R_c \beta \frac{V_{IN} - 0.7}{R_B} \quad \text{--- (1)}$$



If $V_o < 0.2$, then $V_o = 0.2$ (saturation)

(using 1) $V_{IN} < 0.7$ then

$$V_o = V_{CC}$$


(cut off)

If

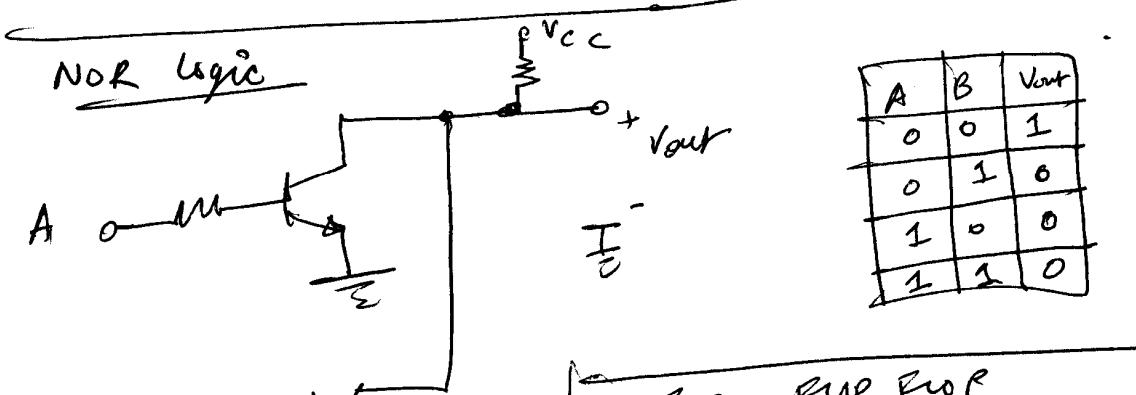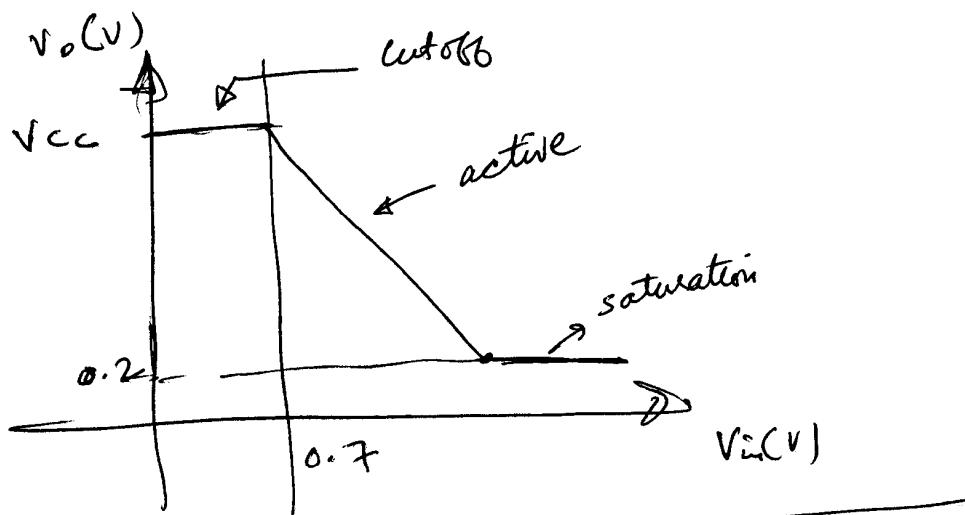


A	B	Vout
0	0	1
0	1	0
1	0	0
1	1	0

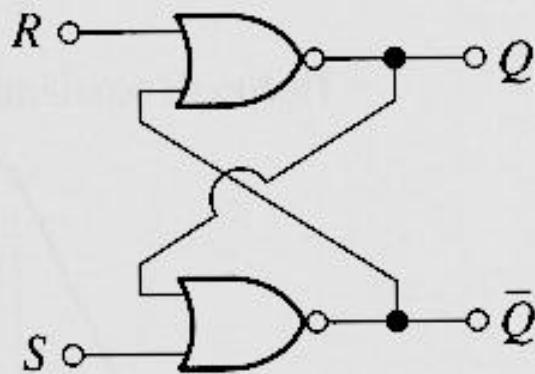PRD PUP PRD
 Q and \bar{Q} opposite logic
 $S \Rightarrow Q=1, R \Rightarrow Q=0$
 $(S, R)=(0, 0)$ keep previous state
 $(S, R)=(1, 1)$ NOT ACCUED.



(a) Logic diagram

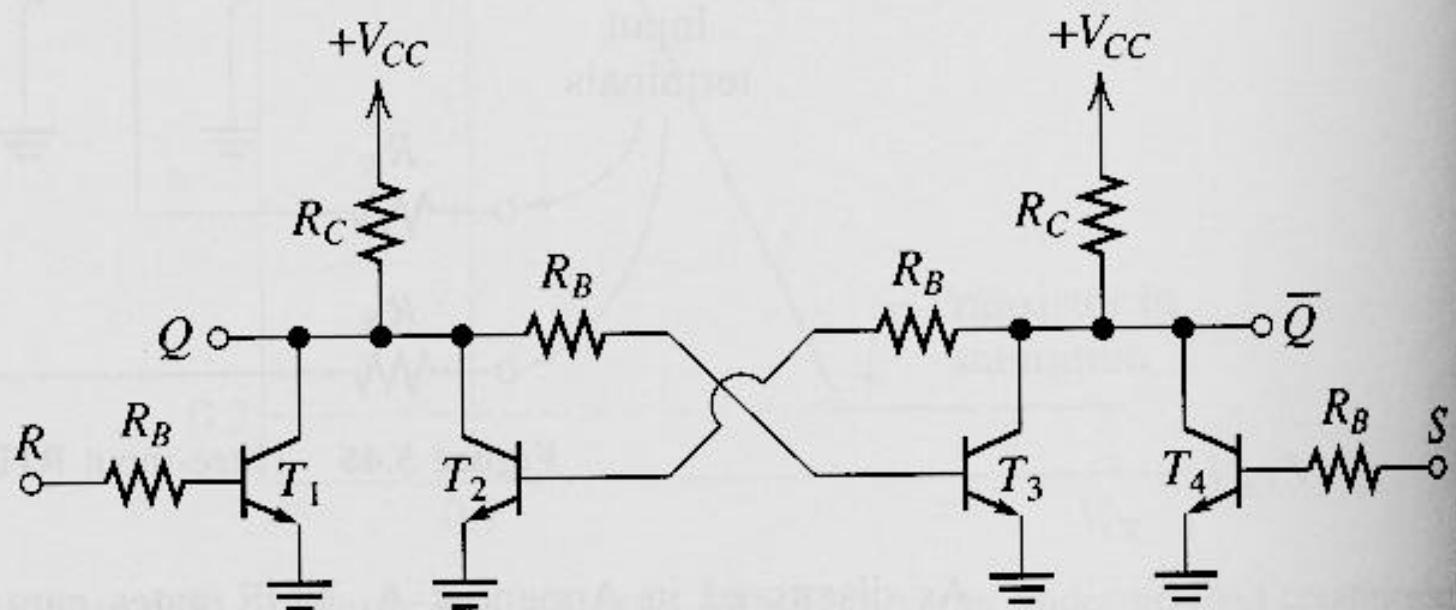

(b) RTL circuit diagram

Figure 5.47 RS flip-flop.