

E8.15 Find V_o in Fig. E8.15.

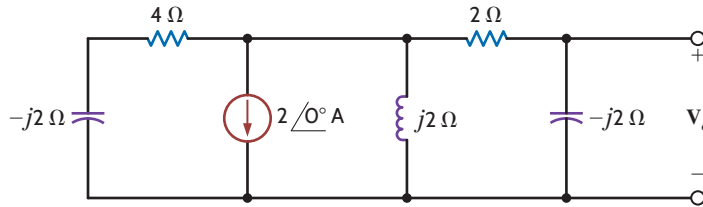


FIGURE E8.15

Answer:

$$V_o = 2.98 \angle -153.43^\circ \text{ V.}$$

E8.16 In the network in Fig. E8.16, V_o is known to be $8 \angle 45^\circ \text{ V}$. Compute V_s .

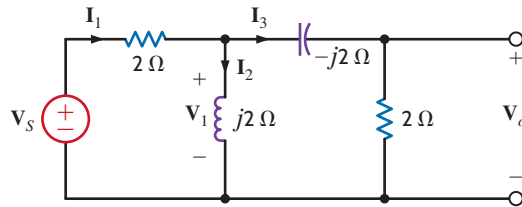


FIGURE E8.16

Answer:

$$V_s = 17.89 \angle -18.43^\circ \text{ V.}$$

8.8 Analysis Techniques

In this section we revisit the circuit analysis methods that were successfully applied earlier to dc circuits and illustrate their applicability to ac steady-state analysis. We will present these techniques through examples in which all the theorems, together with nodal analysis and loop analysis, are used to obtain a solution.

EXAMPLE 8.15

Let us determine the current I_o in the network in Fig. 8.17a using nodal analysis, loop analysis, superposition, source exchange, Thévenin's theorem, and Norton's theorem.

Solution

- Nodal Analysis** We begin with a nodal analysis of the network [see HINT 8.21]. The KCL equation for the supernode that includes the voltage source is

$$\frac{V_1}{1+j} - 2 \angle 0^\circ + \frac{V_2}{1} + \frac{V_2}{1-j} = 0$$

and the associated KVL constraint equation is

$$V_1 + 6 \angle 0^\circ = V_2$$

HINT 8.21

Summing the current, leaving the supernode. Outbound currents have a positive sign.

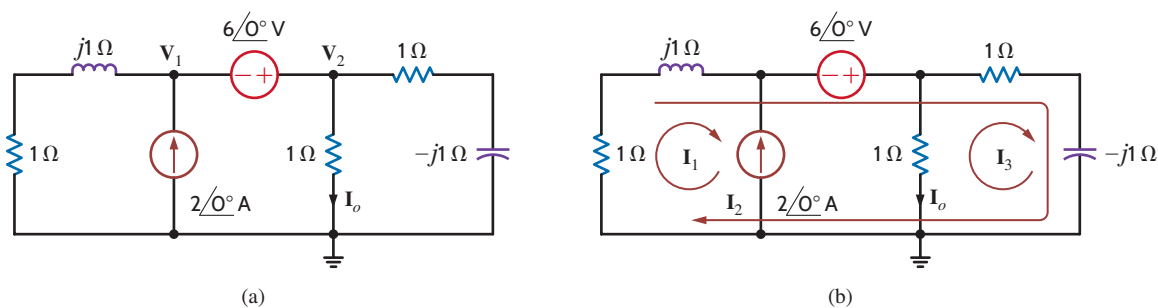


FIGURE 8.17 Circuits used in Example 8.15 for node and loop analysis.

The two equations in matrix form are

$$\begin{pmatrix} 0.5 - 0.5j & 1.5 + 0.5j \\ 1 & -1 \end{pmatrix} \begin{pmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{pmatrix} = \begin{pmatrix} 2 \\ -6 \end{pmatrix}$$

The MATLAB solution is then

```
>> Y = [0.5-0.5j 1.5+0.5j; 1 -1]
Y =
    0.5000-0.5000i    1.5000+0.5000i
    1.0000           -1.0000

>> I = [2; -6]
I =
     2
    -6

>> V = inv(Y)*I
V =
   -3.5000-1.5000i
    2.5000-1.5000i

>> abs (V)
    3.8079
    2.9155

>> 180*phase(v)/pi
Ans =
   -156.8014
   -30.9638
```

And since $\mathbf{I}_0 = \mathbf{V}_2/1$, $\mathbf{I}_0 = 2.9155 \angle -30.9638^\circ$ A

```
>> 180*phase(V)/pi
ans =
   -156.8014
   -30.9638
```

And since $\mathbf{I}_0 = \mathbf{V}_2/1$, $\mathbf{I}_0 = 2.9155 \angle -30.9638^\circ$ A.

HINT 8.22

Just as in a dc analysis, the loop equations assume that a decrease in potential level is + and an increase is -.

2. **Loop Analysis** The network in Fig. 8.17b is used to perform a loop analysis [see HINT 8.22]. Note that one loop current is selected that passes through the independent current source. The three loop equations are

$$\begin{aligned} \mathbf{I}_1 &= -2 \angle 0^\circ \\ 1(\mathbf{I}_1 + \mathbf{I}_2) + j1(\mathbf{I}_1 + \mathbf{I}_2) - 6 \angle 0^\circ + 1(\mathbf{I}_2 + \mathbf{I}_3) - j1(\mathbf{I}_2 + \mathbf{I}_3) &= 0 \\ 1\mathbf{I}_3 + 1(\mathbf{I}_2 + \mathbf{I}_3) - j1(\mathbf{I}_2 + \mathbf{I}_3) &= 0 \end{aligned}$$

Combining the first two equations yields

$$\mathbf{I}_2(2) + \mathbf{I}_3(1-j) = 8 + 2j$$

The third loop equation can be simplified to the form

$$\mathbf{I}_2(1-j) + \mathbf{I}_3(2-j) = 0$$

The equations in matrix form are

$$\begin{bmatrix} 2 & 1-j \\ 1-j & 2-j \end{bmatrix} \begin{bmatrix} \mathbf{I}_2 \\ \mathbf{I}_3 \end{bmatrix} = \begin{bmatrix} \mathbf{I}_2 \\ \mathbf{I}_3 \end{bmatrix} \begin{bmatrix} 8+2j \\ 0 \end{bmatrix}$$

The MATLAB solution is then

```
>> Z = [2 1-j; 1-j 2-j]
Z =
    2.0000           1.0000 - 1.0000i
    1.0000 - 1.0000i    2.0000 - 1.0000i
```

```

>> V = [8+2*j; 0]
V =
    8.0000 + 2.0000i
    0
>> I = inv(Z)*V
I =
    4.5000 - 1.0000i
   -2.5000 + 1.5000i
>> abs (I)
ans =
    4.6098
    2.9155
>> 180*phase(I)/pi
ans =
   -12.5288
   149.0362

```

Therefore, $I_3 = 2.9155/149.0362^\circ$ and $I_0 = -I_3 = 2.9155/-30.9638^\circ$ A.

3. **Superposition** In using superposition, we apply one independent source at a time [see **HINT 8.23**]. The network in which the current source acts alone is shown in **Fig. 8.18a**. By combining the two parallel impedances on each end of the network, we obtain the circuit in **Fig. 8.18b**, where

$$Z' = \frac{(1+j)(1-j)}{(1+j) + (1-j)} = 1 \Omega$$

Therefore, using current division,

$$I'_0 = 1 \angle 0^\circ \text{ A}$$

The circuit in which the voltage source acts alone is shown in **Fig. 8.18c**. The voltage V''_1 obtained using voltage division is

$$\begin{aligned} V''_1 &= \frac{(6 \angle 0^\circ) \left[\frac{1(1-j)}{1+1-j} \right]}{1+j + \left[\frac{1(1-j)}{1+1-j} \right]} \\ &= \frac{6(1-j)}{4} \text{ V} \end{aligned}$$

and hence,

$$I''_0 = \frac{6}{4}(1-j) \text{ A}$$

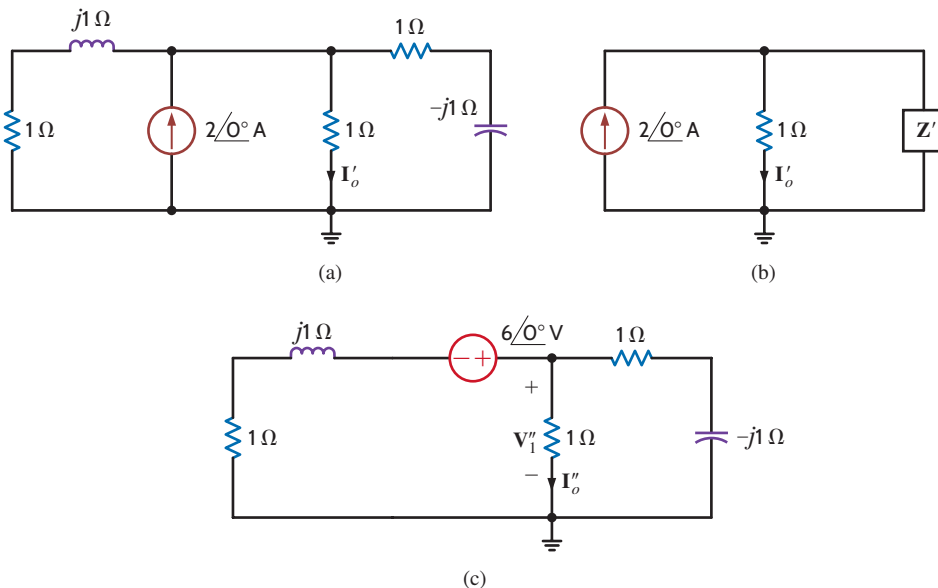


FIGURE 8.18 Circuits used in Example 8.15 for a superposition analysis.

HINT 8.23

In applying superposition in this case, each source is applied independently, and the results are added to obtain the solution.

HINT 8.24

In source exchange, a voltage source in series with an impedance can be exchanged for a current source in parallel with the impedance and vice versa. Repeated application systematically reduces the number of circuit elements.

Then

$$I_o = I'_o + I''_o = 1 + \frac{6}{4}(1 - j) = 2.9155 \angle -30.9638^\circ \text{ A.}$$

4. **Source Exchange** As a first step in the source exchange approach, we exchange the current source and parallel impedance for a voltage source in series with the impedance, as shown in Fig. 8.19a [see HINT 8.24].

Adding the two voltage sources and transforming them and the series impedance into a current source in parallel with that impedance are shown in Fig. 8.19b. Combining the two impedances that are in parallel with the 1-Ω resistor produces the network in Fig. 8.19c, where

$$Z = \frac{(1 + j)(1 - j)}{1 + j + 1 - j} = 1 \Omega$$

Therefore, using current division,

$$I_o = \left(\frac{8 + 2j}{1 + j} \right) \left(\frac{1}{2} \right) = \frac{4 + j}{1 + j} = 2.9155 \angle -30.9638^\circ \text{ A}$$


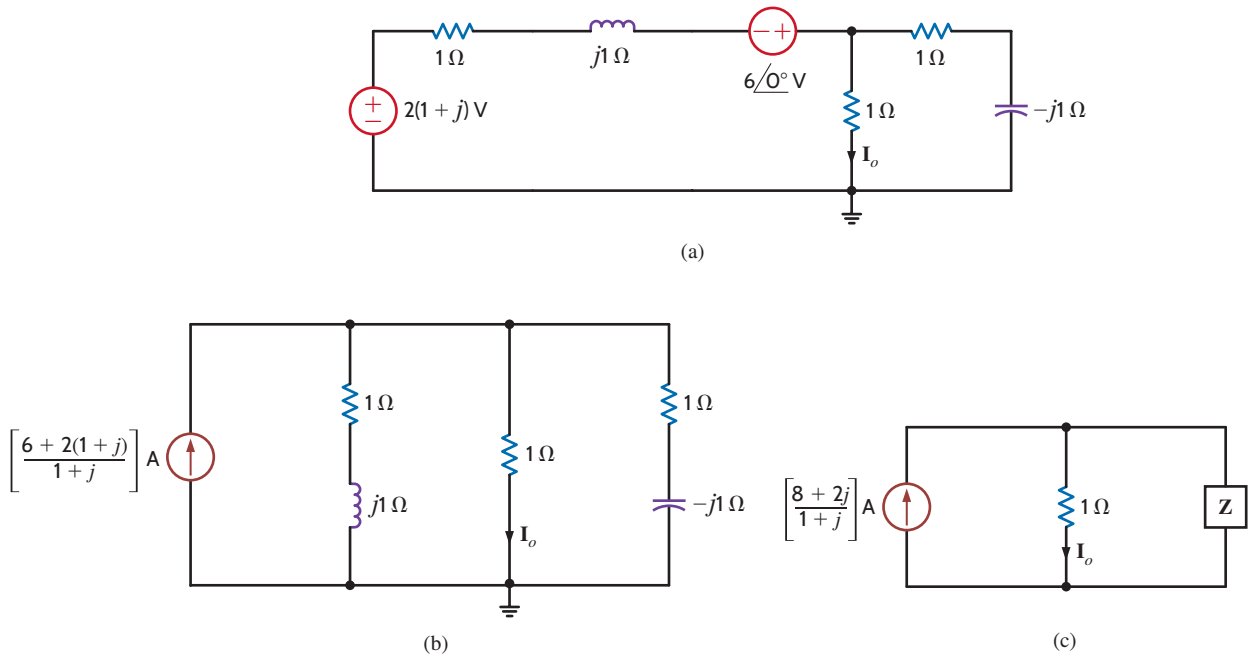


FIGURE 8.19 Circuits used in Example 8.15 for a source exchange analysis.

HINT 8.25

In this Thévenin analysis,

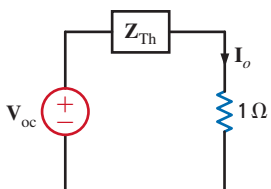1. Remove the 1-Ω load and find the voltage across the open terminals, V_{oc} .
2. Determine the impedance Z_{Th} at the open terminals with all sources made zero.
3. Construct the following circuit and determine I_o .



5. **Thévenin Analysis** In applying Thévenin's theorem to the circuit in Fig. 8.17a, we first find the open-circuit voltage, V_{oc} , as shown in Fig. 8.20a [see HINT 8.25]. To simplify the analysis, we perform a source exchange on the left end of the network, which results in the circuit in Fig. 8.20b. Now using voltage division,

$$V_{oc} = [6 + 2(1 + j)] \left[\frac{1 - j}{1 - j + 1 + j} \right]$$

or

$$V_{oc} = (5 - 3j) \text{ V}$$

The Thévenin equivalent impedance, Z_{Th} , obtained at the open-circuit terminals when the current source is replaced with an open circuit and the voltage source is replaced with a short circuit, is shown in Fig. 8.20c and calculated to be

$$Z_{Th} = \frac{(1 + j)(1 - j)}{1 + j + 1 - j} = 1 \Omega$$

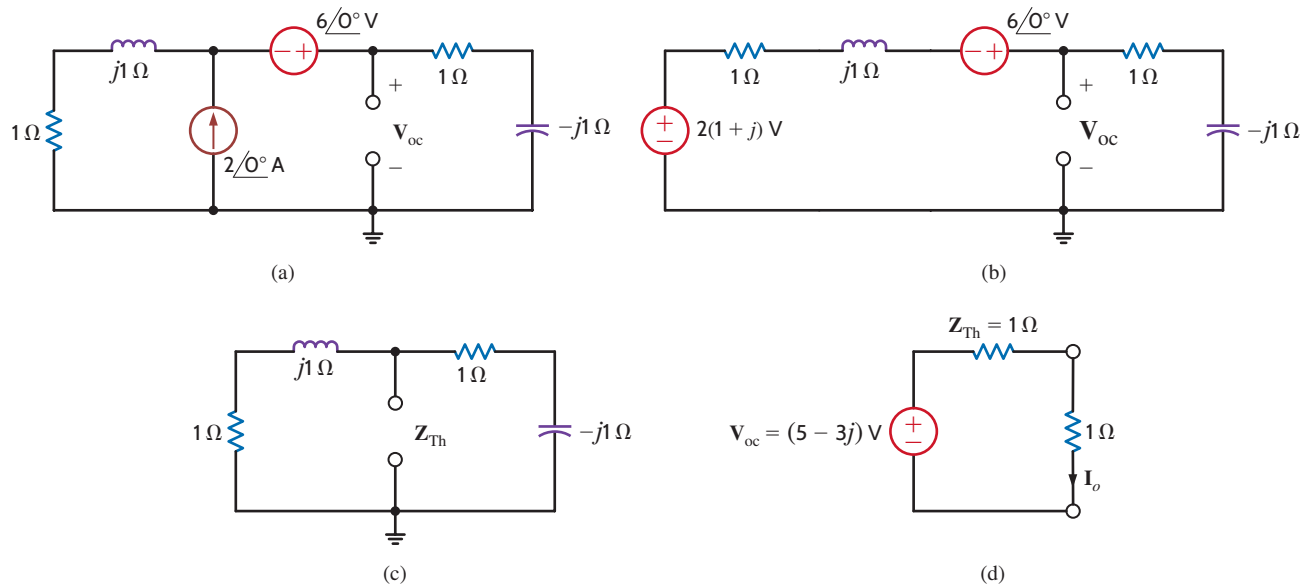


FIGURE 8.20 Circuits used in Example 8.15 for a Thévenin analysis.

Connecting the Thévenin equivalent circuit to the 1-Ω resistor containing I_o in the original network yields the circuit in **Fig. 8.20d**. The current I_o is then

$$I_o = 2.9155 \angle -30.9638^\circ \text{ A}$$

6. Norton Analysis Finally, in applying Norton's theorem to the circuit in **Fig. 8.17a**, we calculate the short-circuit current, I_{sc} , using the network in **Fig. 8.21a** [see **HINT 8.26**]. Note that because of the short circuit, the voltage source is directly across the impedance in the left-most branch. Therefore,

$$I_1 = \frac{6 \angle 0^\circ}{1 + j}$$

Then, using KCL,

$$\begin{aligned} I_{sc} &= I_1 + 2 \angle 0^\circ = 2 + \frac{6}{1 + j} \\ &= \left(\frac{8 + 2j}{1 + j} \right) \text{ A} \end{aligned}$$

The Thévenin equivalent impedance, Z_{Th} , is known to be 1 Ω and, therefore, connecting the Norton equivalent to the 1-Ω resistor containing I_o yields the network in **Fig. 8.21b**. Using current division, we find that

$$\begin{aligned} I_o &= \frac{1}{2} \left(\frac{8 + 2j}{1 + j} \right) \\ &= 2.9155 \angle -30.9638^\circ \text{ A} \end{aligned}$$

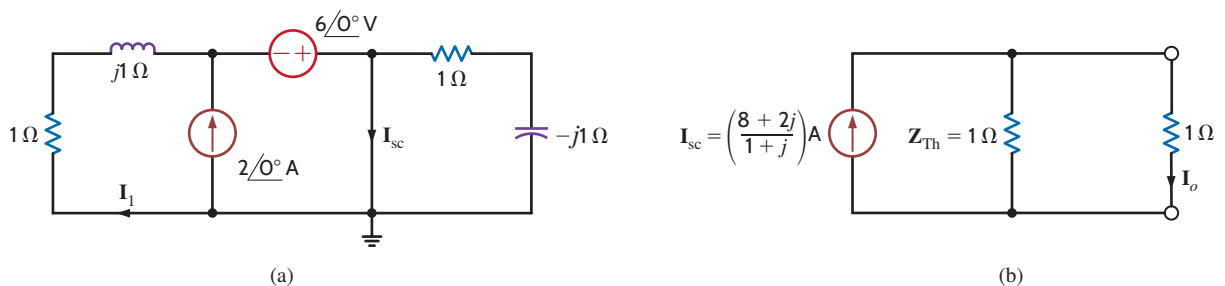


FIGURE 8.21 Circuits used in Example 8.15 for a Norton analysis.

HINT 8.26

In this Norton analysis,

1. Remove the 1-Ω load and find the current I_{sc} through the short-circuited terminals.
2. Determine the impedance Z_{Th} at the open load terminals with all sources made zero.
3. Construct the following circuit and determine I_o .

